

Prob.1 For a circuit as shown in Figure 1, answer the followings.

- (a) Find a Thevenin's equivalent circuit with respect to terminal a-b.(8 pts)
 (b) If the box X represents a passive element, and its i-v characteristic is expressed as follows. Please calculate v and i. (7 pts)

$$i = \begin{cases} 0 & ; v \leq 2 \text{ volts} \\ \frac{1}{5}(v - 2) & ; v > 2 \text{ volts} \end{cases}$$

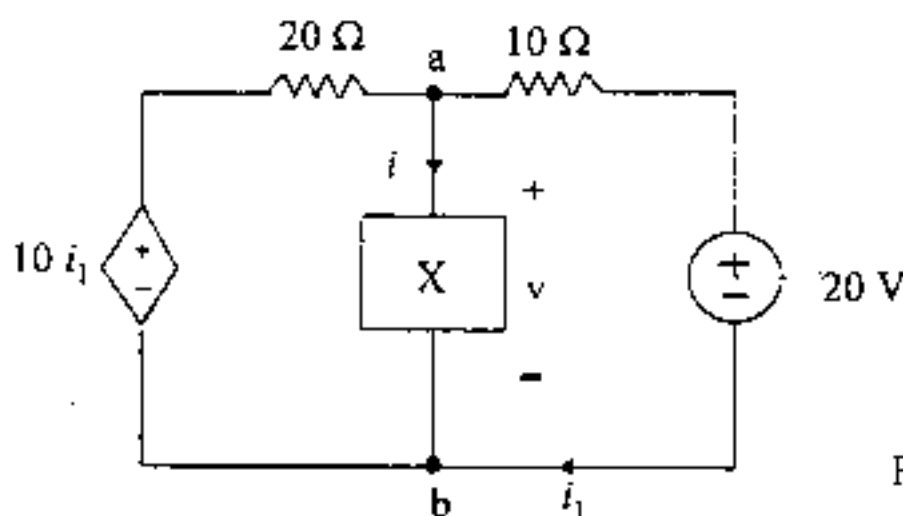


Figure 1

Prob.2 For a circuit as shown in Figure 2, assuming that it has reached sinusoidal steady state, calculate the followings.

- (a) If a passive load is connected to terminal x-y, what is(are) passive element(s) to be used to achieve a maximum average power transfer.(5 pts)
 (b) What can the maximum average power be transferred in watts?(5 pts)
 (c) Based on (b), calculate the effective power being consumed by the 2Ω-resistor.(5pts)
 (d) Based on (b), calculate the real power being absorbed(or delivered) by the 0.8 V_{xy} dependent source.(5pts)

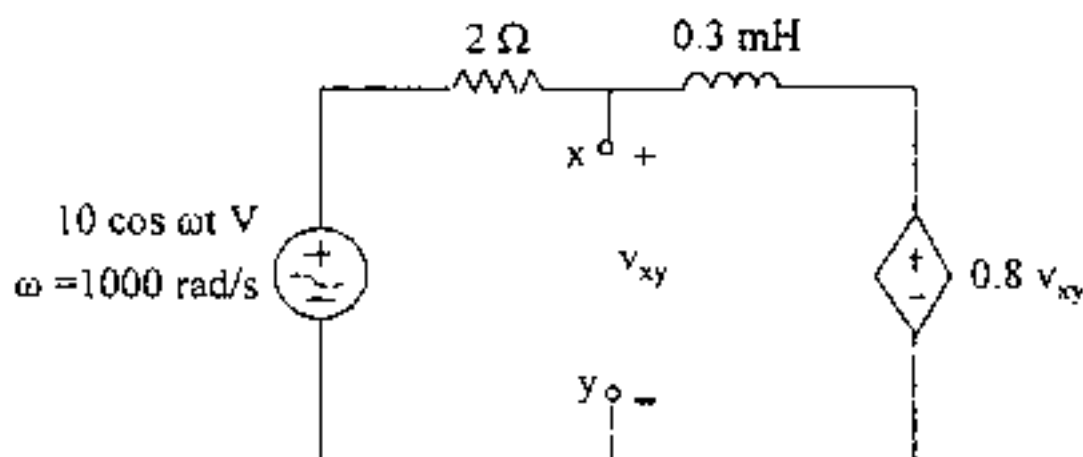


Figure 2

八十七學年度 動力機械 系(所) 乙 組碩士班研究生入學考試

電工學

科號 2602 共 4 頁第 2 頁 *請在試卷【答案卷】內作答

Prob.3 For a switching circuit shown in Figure 3(a), answer the following questions, and provide any assumption needed to justify your reasoning and/or calculations.

- (a) If now, you are given $V_s = 12$ volts, $L = 0.1$ H, $C = 1000 \mu\text{F}$, $T_{\text{ON}} = 8$ ms, $T_{\text{OFF}} = 2$ ms, calculate ΔI as shown in Figure 3(b) in Amps.(4 pts)
- (b) With the given waveforms of the switch S and the inductor current I_L . Plot the corresponding waveforms of V_L and I_D versus time, respectively.(6 pts)
- (c) If the load is purely resistive and $R_L = 1\text{K}\Omega$, plot I_o versus time.(5 pts)

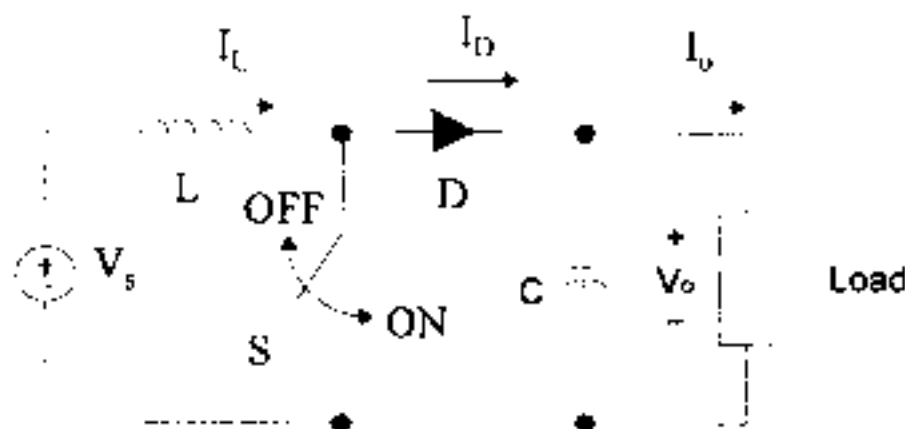


Figure 3(a)

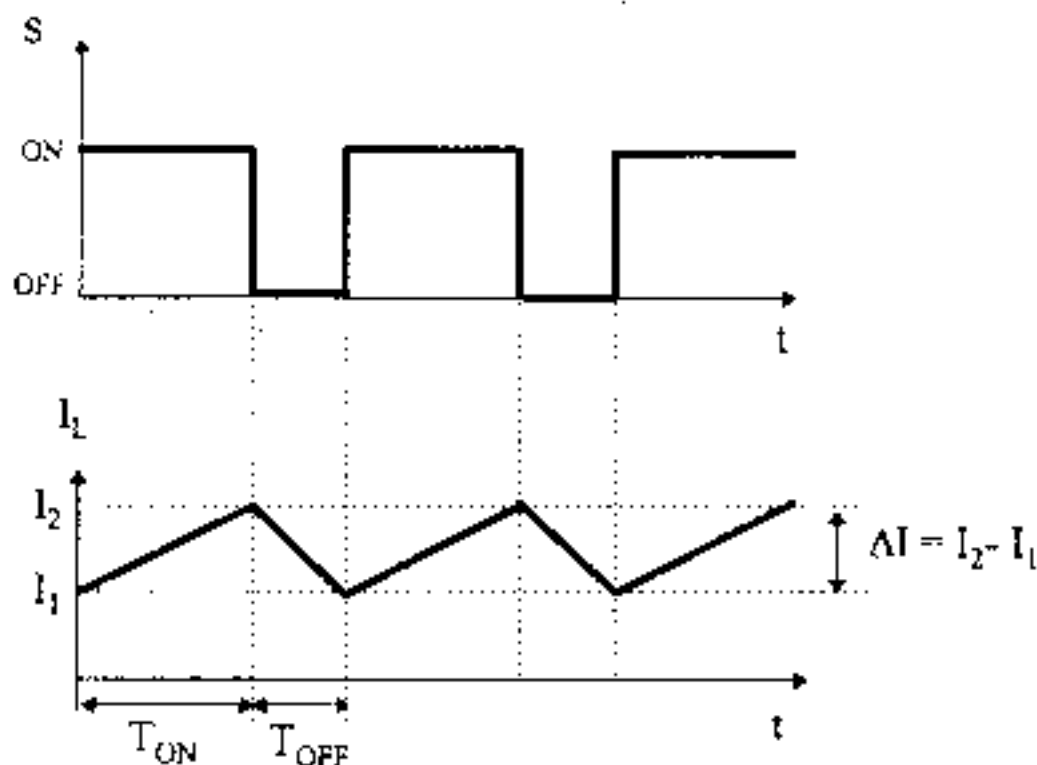


Figure 3(b)

八十七學年度 動力機械 系(所) 乙 組碩士班研究生入學考試

電工學

科號 2602 共 4 頁第 3 頁 *請在試卷【答案卷】內作答

Prob.4 Please choose the items from (a) to (k) which describe the terminology from (1) to (5) given as follows. (Note: in multiple choices) (5 pts)

- (1) Gallium Arsenide. (2) Bridge Rectifier. (3) Miller Capacitance.
 (4) Schmitt Triggering Circuit. (5) Glitches.

- (a) Semiconductor for opto-electronic devices.
 (b) Commonly found in circuits with large capacitors.
 (c) Threshold voltage larger than 0.7 volt.
 (d) Reverse-biased junction contributes the effect.
 (e) Group III-V compound.
 (f) Usually need to know the gain value.
 (g) Immune to noisy signal.
 (h) Digital circuits.
 (i) Unexpected signals.
 (j) Diode laser.
 (k) Implemented by operational amplifiers.

Prob.5 Sketch v_o versus time for the circuit shown in Fig. 4. Assume $V_f = 0.7$ V and the RC time constant is large compared to the input frequency. (5 pts)

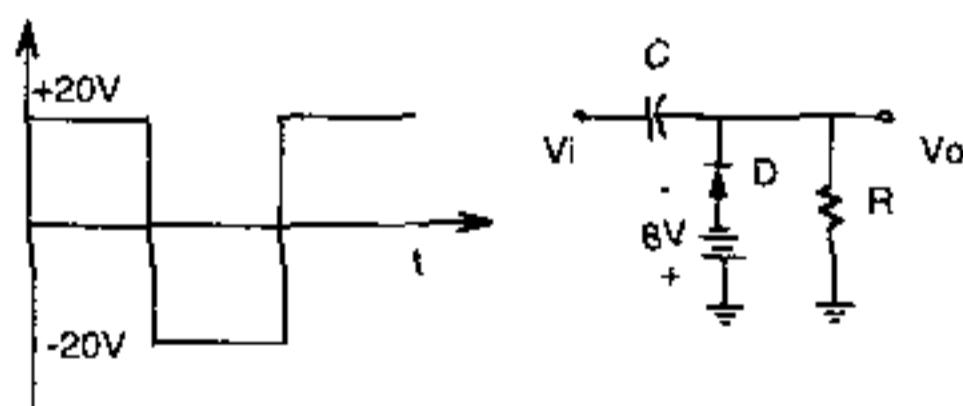


Figure 4

Prob.6 Design a 3-bit counter circuit which uses JK Flip-Flop according to the following steps. (15 pts)

- (a) Set the counter go with the sequence as 000,001,010,011,100; then repeat again.
 (b) List the truth table of the JK Flip-Flop.
 (c) Simplify the state logic by the K-map.
 (d) Draw the circuit diagram.
 (e) Verify the circuit by timing diagram.

Prob.7 If $f(X,Y,Z)=\Sigma(0,2,4,5,7)$;

- (a) prove that $f(X,Y,Z)=\Pi(1,3,6)$. (3 pts)
- (b) implement $f(X,Y,Z)$ by making use of a 3 to 8 decoder and a OR logic IC. (2 points)

Prob.8 For the Log Amplifier implemented with a diode as shown in Figure 5,

- (a) derive the gain A_v . (7 pts)
 - (b) what happens if v_i goes negative? Please explain. (3 pts)
- (Hint: $i_D = I_S(e^{v_D/V_T} - 1)$)

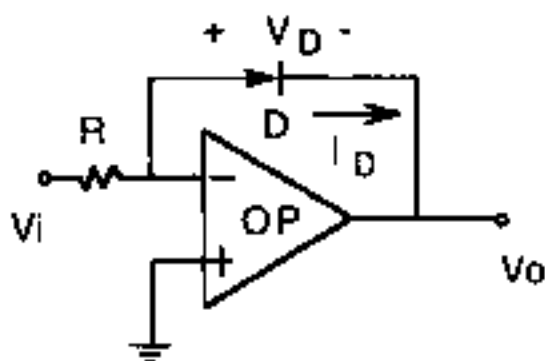


Figure 5

Prob.9 For a cascode BJT amplifier circuit as shown in Figure 6, if Q_1 and Q_2 are the same BJT with the hybrid- π parameters r_i and g_m .

- (a) Please derive the voltage gain A_v . (8 pts)
- (b) Please write down at least one of the advantages of the circuits. (2 pts)

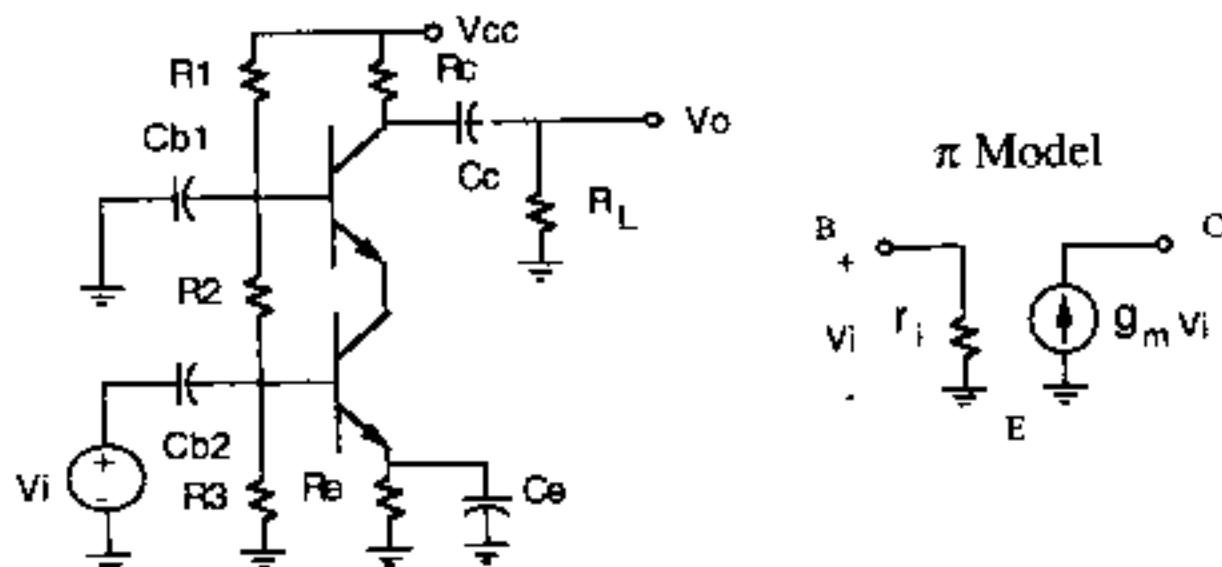


Figure 6