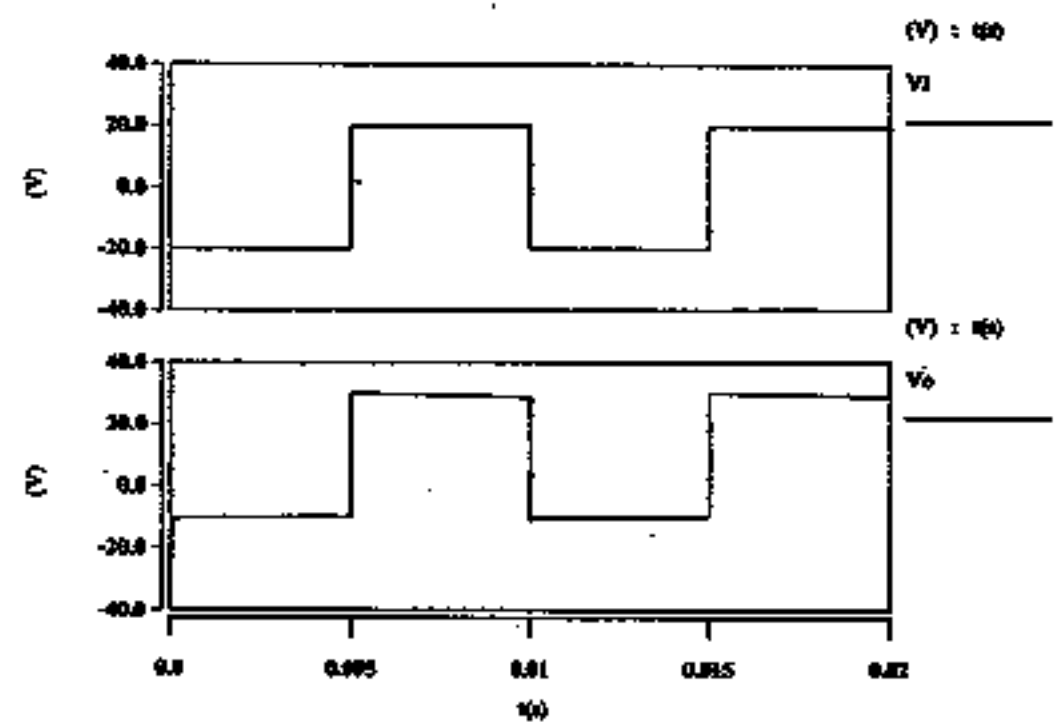


- (1) Explain the following terminology in the sense of Logic Design:
- (a) Finite State Machine. (2%)
 - (b) Flip-flop. (2%)
 - (c) Hazard. (2%)
 - (d) Sequential Logic. (2%)


(2) Based on the terminological words in the following items from (a) to (j), please choose the closest descriptions numbered from (1) to (10). (10%)

- | | |
|---------------------------------|---|
| (a) Photo diode. | (1) Using p and n channel on the same wafer. |
| (b) Diffusion current. | (2) With very large impedance on both inputs. |
| (c) Emitter follower amplifier. | (3) Provide super high current gain. |
| (d) Early effect. | (4) Parasitic capacitance between B and C. |
| (e) Darlington transistor. | (5) Controllable reverse junction current. |
| (f) CMOS technology. | (6) Contribute to the output resistance. |
| (g) Common rejection. | (7) Voltage gain is smaller than unity. |
| (h) Instrumentation amplifier. | (8) Controlled by gate voltage level. |
| (i) Miller capacitance. | (9) Due to difference in carrier concentration. |
| (j) Pinch-off effect. | (10) Ability to reduce common mode signals. |


(3) Design a diode clamper to generate the output V_o from the input V_i as shown in the following plots if the V_f of the diode is assumed to be 0 volt. Hint: the circuit must have a diode, a capacitor, a resistor, and a voltage source. (10 %)



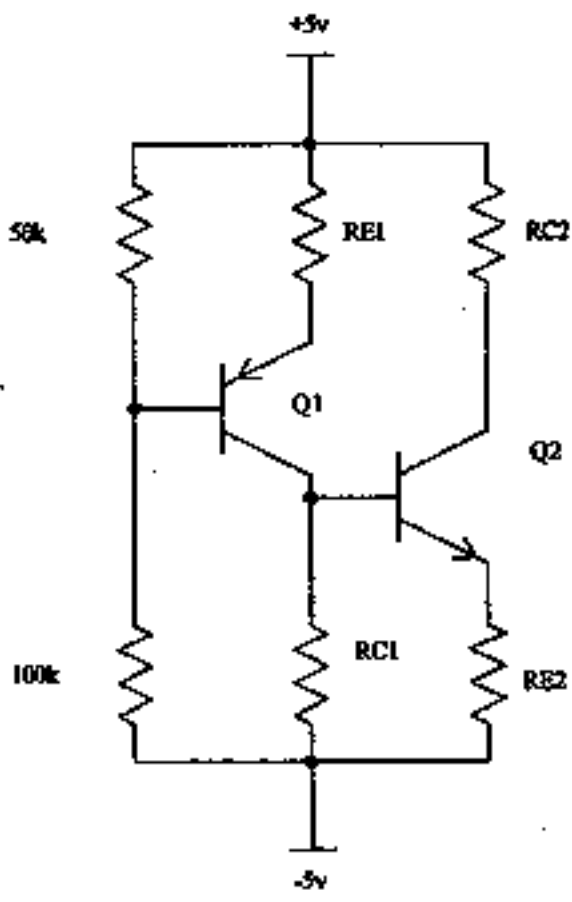
(4) For the transistor amplifier shown in the following figure, the parameters of the transistor are: $\beta=100$, $V_{BE(on)}=V_{EB(off)}=0.7$ V. Determine the R_{C1} , R_{C2} , R_{E1} , and R_{E2} such that $I_{C1}=I_{C2}=1$ mA and $V_{CEQ1}=3.5$ V and $V_{CEQ2}=4.0$ V. (10 %)



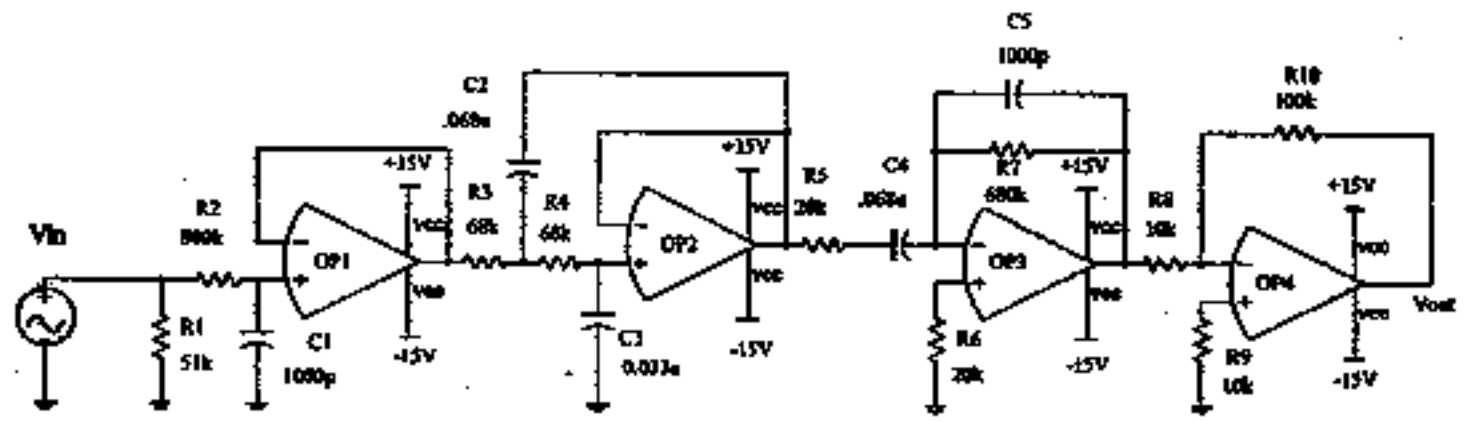(5) For the given signal conditioning circuit based upon four operational amplifiers (OP), (a) please describe the function of each OP in the circuit. (8%) (b) What is the transfer function of the given circuit? (2%) Hint: you can guess it by making use of reasonable assumptions.



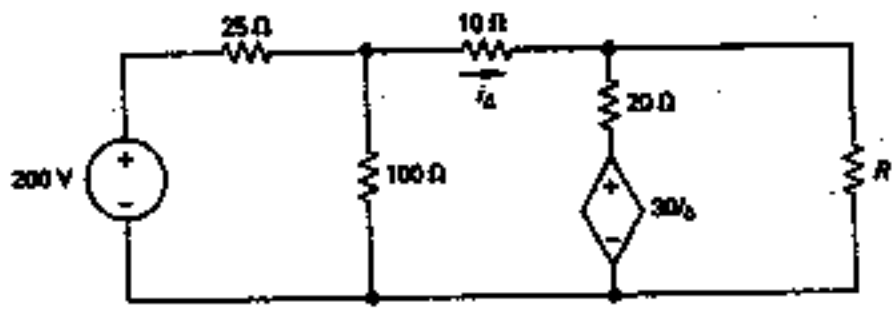- (6) When an ammeter is used to measure the current through the resistor $R = 2 \Omega$ in the circuit shown in the following figure, it read 10 A. What is the resistance of the ammeter?
 (15%)




- (7) The circuit shown in the following figure is in the steady state before the switch closed. Assume that there is no energy stored in the capacitor and inductor initially.

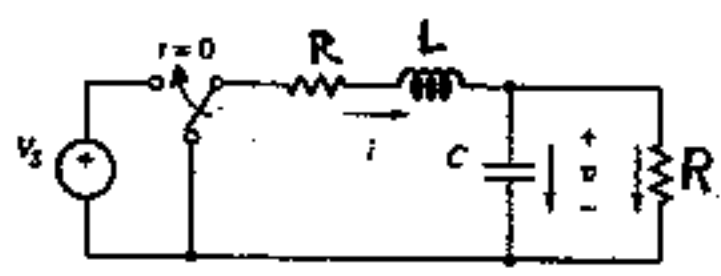
- (a) Derive the differential equation for the voltage (v) across the capacitor when the switch is closed at $t = 0$. (5%)
 (b) Use the results in part (a), if the voltage response in the capacitor, $C = 1 \mu F$, due to the step function V_s is

$$v(t) = 5 \left\{ 1 - Ae^{-t} \cos(t - \phi) \right\} \text{ V.}$$

Find the values of L , R , V_s , A , and ϕ (in degree). (10%)



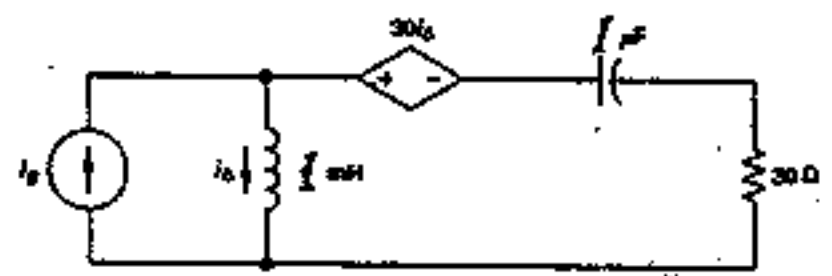- (8) Find the average power dissipated in the 30Ω resistor in the circuit seen in the following figure if $i_g = 10 \cos(10,000t)$ A. (10%)



(9) Given a four-input Boolean function, $f(A,B,C,D) = \sum m(1, 2, 4, 7, 8, 11, 13, 14)$,

(a) Minimize the product of sums form for the function. (4%)

(b) Implement the function using a 4:1 multiplexer where variables A and B are selected as the control inputs. (8%)