

九十一學年度 動力機械工程 系(所) 乙 組碩士班研究生招生考試

科目 電工學 科號 1402 共 4 頁第 1 頁 *請在試卷【答案卷】內作答

- (1) A test is performed on a passive circuit in order to understand its characteristics. In this test, a 1-volt, 1 Hz sinusoidal voltage (v) is connected as the input to the circuit; and, the current (i) is measured. The measured waveforms for v and i are shown in Fig. 1 below. It is known that the circuit is either a RL or a RC circuit. Please determine
- the equivalent resistance of the circuit (5 points);
 - the equivalent inductance (or capacitance) of the circuit (5 points).

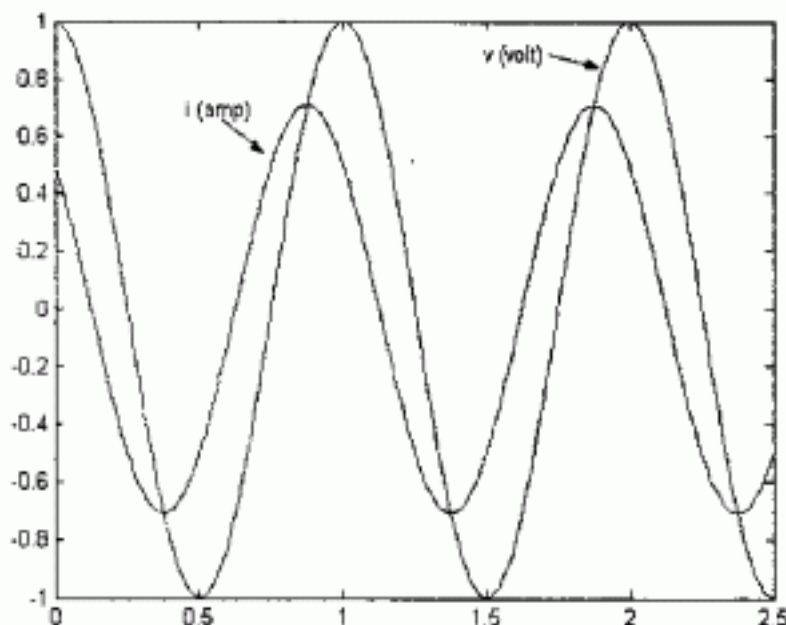
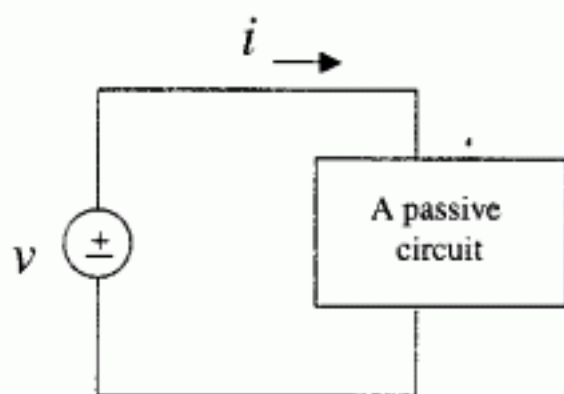


Fig. 1

- (2) When connected to a variable resistor, a power supply exhibits the voltage-resistance characteristics as shown in Fig. 2. Please determine the equivalent circuit of the power supply. (6 points)

九十一學年度 動力機械工程系(所) 乙 組碩士班研究生招生考試

科目 電工學 科號 1402 共 4 頁第 2 頁 *請在試卷【答案卷】內作答

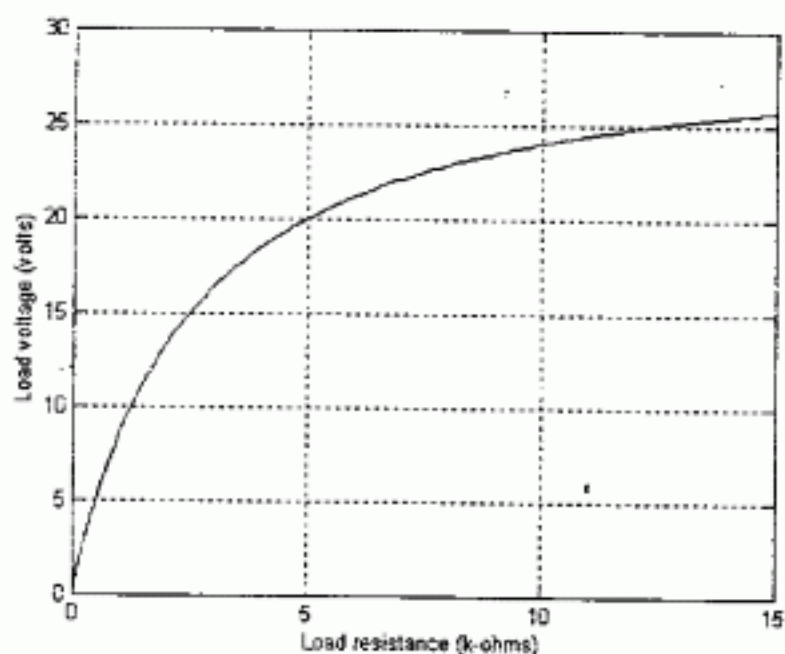


Fig. 2

- (3) In the following *RLC* circuit as shown in Fig. 3, assume that the input is $v_i = \sin(\omega t)$ and the output v_o equals to $V \sin(\omega t + \phi)$ at steady state.
- Determine the amplitude (V) and the phase (ϕ) as functions of ω . Plot respectively V v.s. ω and ϕ v.s. ω . (10 points)
 - From the results in (a), determine the frequency ω_0 where V achieves its maximum V_{\max} and $V_{\max} = ?$ (9 points)
 - Determine the two frequencies (ω_1, ω_2) $V = \frac{1}{\sqrt{2}} V_{\max}$. (8 points)
 - Compute values for R and L to yield a circuit with $\omega_0 = 5\text{kHz}$ and $\omega_2 - \omega_1 = 200\text{Hz}$ using a $5\mu\text{F}$ capacitor. (7 points)

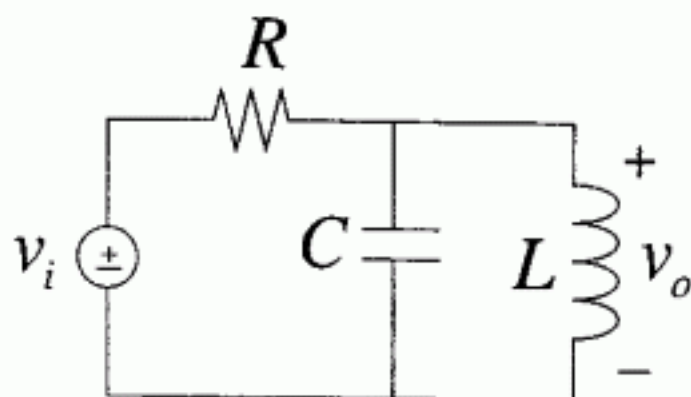


Fig. 3

九十一學年度 動力機械工程系(所) 乙 組碩士班研究生招生考試

科目 電工學 科號 1402 共 4 頁第 3 頁 *請在試卷【答案卷】內作答

- (4) A pn junction diode built in silicon has the following parameters, which represent data for the diode and silicon at room temperature.

Bandgap energy of silicon = 1.1 eV; Intrinsic free carrier density in silicon = $1.1(10^{10}) \text{ cm}^{-3}$; N_A (p side) = 10^{18} cm^{-3} ; N_D (n side) = 10^{17} cm^{-3}

- (a) Determine the built-in potential offset (3 points).
 (b) Determine the depletion length both in n-material and in p-material, respectively (4 points).
 (c) Sketch the energy band profile for the pn junction diode and label the energy bandgap, depletion region and built in potential (5 points).
- (5) Calculate the resistance of a layer of n-type Si which is doped with donor species at a concentration of 10^{17} cm^{-3} , is 10^{-4} cm^2 in area and $5 \mu\text{m}$ thick. Assume an electron mobility of $750 \text{ cm}^2/\text{volt}\cdot\text{sec}$. This film might represent the major contribution of the series resistance of a pn junction diode. If so, at what forward bias current would the series resistance begin to have an effect on the diode's voltage drop (i.e. when is $r_d < R_{\text{series}}$)? Remember that at large forward bias $\eta \cong 1$ (12 points).
 [Hint: Equations may be used in the calculations.]

$$n_i^2 = N_c N_v \exp\left(\frac{-E_g}{kT}\right)$$

$$C = \left[\frac{q\epsilon_s}{2(\phi_i - V_a) \left(\frac{1}{N_a} + \frac{1}{N_d} \right)} \right]^{1/2}$$

$$L_D = \left[\frac{\epsilon_s kT}{q^2 N_d} \right]^{1/2}$$

$$x_n + x_p = \left[2 \frac{\epsilon_s}{q} (\phi_i - V_a) \left(\frac{1}{N_a} + \frac{1}{N_d} \right) \right]^{1/2}$$

$$\phi_n = \frac{kT}{q} \ln \frac{N_d}{n_i}$$

$$\bar{J}_{nx} = q\mu_n n \bar{E}_x + q\bar{D}_n \frac{dn}{dx}$$

- (6) Which bias applied in a MOSFET has the strongest influence on "channel length modulation"? Why does the channel length modulation result in Early effect? (6 points)
- (7) When designing the output stage of a power amplifier, Darlington Configuration has commonly employed for circumventing the low dc β problem.
- (a) Please draw a schematic figure to show the Darlington pairs consisting of two npn bipolar transistors (4 points).
- (b) Derive the combined current gain for the Darlington pairs if the two npn transistors are assumed to have the same dc β (4 points).

國 立 清 華 大 學 命 題 紙

九十一學年度 動力機械工程系(所) 乙 組碩士班研究生招生考試

科目 電工學 科號 1402 共 4 頁第 4 頁 *請在試卷【答案卷】內作答

- (8) In most op-amp circuits, the linear circuits are based upon negative feedback analysis when details of the circuits are designed.
- (a) Please write down the ideal op-amp characteristics that can be concluded from the feedback theory (4 points).
 - (b) Draw the inverting, non-inverting, and difference amplifiers based upon the feedback concept with ideal op-amps (4 points).
 - (c) When non-linear components, such as diodes, are used in the design, what are the possible functions of the op-amp circuits? Please draw at least one op-amp circuit and describe the results. (4 points)