

九十三學年度 動機 系(所) 乙 組碩士班入學考試

科目 電路學及電子學 科號 1602 共 4 頁第 1 頁 \*請在試卷【答案卷】內作答

1. A fully loaded 5-hp induction motor operates at 70 percent efficiency and a lagging power factor of 0.8. (One horsepower is approximately 745.7 W).
  - (a) Find the average power and the reactive power delivered to the motor. (4%)
  - (b) By what amount should the reactive power be decreased in order to achieve a power factor of at least 0.95. (4%)
  - (c) It is decided to raise the power factor to 0.95 lagging by placing capacitance in parallel with the power line. Find the value of  $C$  required if the line voltage equals 480V rms and  $f = 60\text{Hz}$ . (6%)

2. Fig 1 shows a Wheatstone bridge

- (a) Prove that the output voltage  $E_0$  is proportional to the resistance change

$$\delta R \text{ if } \frac{\delta R}{R} \ll 1. \text{ Also find the proportional constant. (5\%)}$$

- (b) Design a circuit which can measure an inductance change. (Hint: Use an AC source as the bridge input and replace the resistors by appropriate electrical elements) (7%)

 


Fig. 1

3. If the switch in Fig. 2 has been closed for a long time before  $t = 0$  but is open at  $t = 0$ , determine
  - (a) the characteristic equation of the circuit, (4%)
  - (b)  $i_x$  and  $v_R$  for  $t > 0$ . (8%)

九十三學年度 動機 系(所) 乙 組碩士班入學考試

科目 電路學及電子學 科號 1602 共 4 頁第 2 頁 \*請在試卷【答案卷】內作答

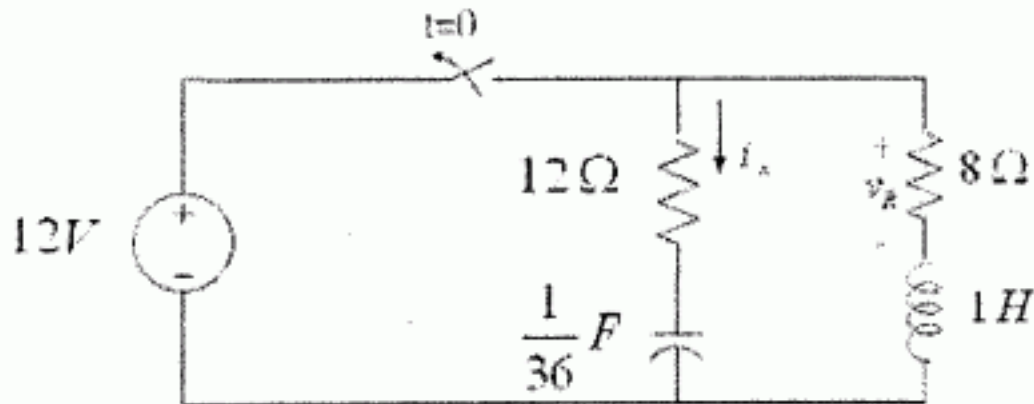


Fig. 2

4. For the circuit in Fig. 3, find the frequency response between  $V_i$  and  $V_o$ . Also draw the corresponding magnitude and phase plots. (12%)

 


Fig. 3

5. Design a diode clamper to generate the output  $v_o$  from the input  $v_i$  shown in the figure if (a)  $V_T=0$ , and (b)  $V_T=0.7V$ . (10%)

九十三學年度 動機 系(所) 乙 組碩士班入學考試

科目 電路學及電子學 科號 1602 共 4 頁第 3 頁 \*請在試卷【答案卷】內作答

 


Fig. 4

6. Design a pnp common-emitter circuit such that  $I_{BQ}=15\mu\text{A}$  and  $V_{ECQ}=2.5\text{V}$  given the following parameters  $V_{BB}=2.5\text{V}$ ,  $V_{CC}=5\text{V}$ , and  $\beta_F=80$ . (10%)

 


Fig. 5

7. For the circuit in the figure, the transistor parameters are:  $K_n=0.5\text{mA/V}^2$ ,  $V_{TN}=2\text{V}$ , and  $\lambda=0$ . Determine the maximum value of  $C_L$  such that the bandwidth is at least  $BW=5\text{MHz}$ . State any approximations or assumptions that you make. (15%)

九十三學年度 動機 系(所) 乙 組碩士班入學考試

科目 電路學及電子學 科號 1602 共 4 頁第 4 頁 \*請在試卷【答案卷】內作答

 


Fig. 6

8. For the amplifier in the figure, determine
- the ideal closed-loop voltage gain (5%)
  - the actual closed-loop voltage if the open-loop gain is  $A_{od}=150,000$  (5%)
  - the open-loop gain such that the actual closed-loop gain is within 1% of the ideal (5%)

 


Fig. 7