

國立清華大學命題紙

96 學年度 動力機械工程學系 乙 (電機控制) 組 碩士班入學考試

科目 電路學及電子學 科目代碼 1102 共 4 頁 第 1 頁 \*請在【答案卷內】內作答

1. Consider a circuit shown below. Assume that the switch  $K_1$  has contacted point A for a long time and switch  $K_2$  is open.  $R$ ,  $L$  and  $C$  represent the resistance, the inductance and the capacitance respectively.

(a) Find  $V_C$ . (5%)

(b) If  $K_1$  is switched to point B at  $t = 0$  and  $K_2$  is still open, find  $v(t)$  for  $t \geq 0$ . (5%)

(c) If  $K_1$  is switched to point B at  $t = 0$  and  $K_2$  is closed at the same time, draw roughly the possible waveforms of  $v(t)$  for  $t \geq 0$ . (5%)

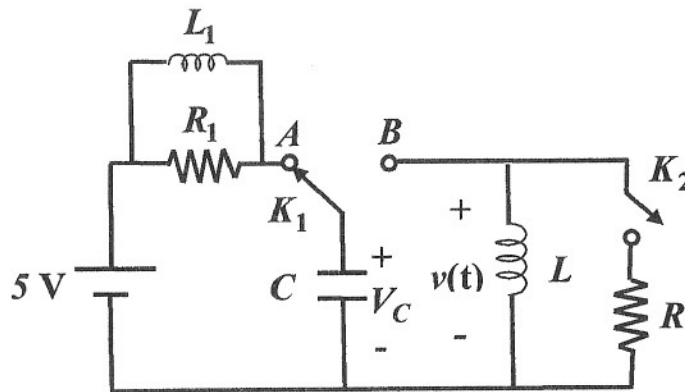


Figure 1

2. Assume that the following two circuits as shown in Fig. 2 are equivalent.

(a) Find  $V_{TH}$  and  $R_{TH}$ . (10%)

(b) Prove that the circuit has delivered maximum power to  $R$  when  $R = R_{TH}$ . (5%)

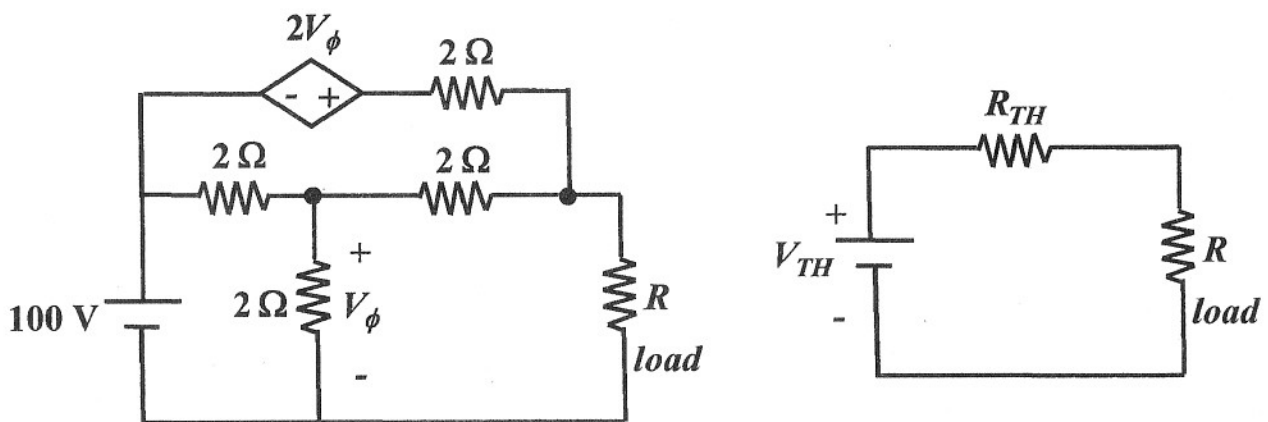


Figure 2

國立清華大學命題紙

96學年度 動力機機工程學系 乙(電機控制)組 碩士班入學考試

科目 電路學及電子學 科目代碼 1102 共 4 頁 第 2 頁 \*請在【答案卷內】內作答

3. Consider a circuit shown in Fig. 3A. Fig. 3B is the phasor-domain equivalence circuit of Fig. 3A.

(a) Find  $I_S$ ,  $Z_{R1}$ ,  $Z_{R2}$ ,  $Z_L$  and  $Z_C$  in Fig. 3B. (5%)

(b) Use the values of (a) to find the matrix  $A$  and the vector  $C$  in the following node-voltage equation

$$A \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = C$$

where  $V_1$  and  $V_2$  in Fig. 3B are phasors of node voltage. (10%)

(c) Find  $i(t)$  when the circuit is in sinusoidal steady state. (5%)

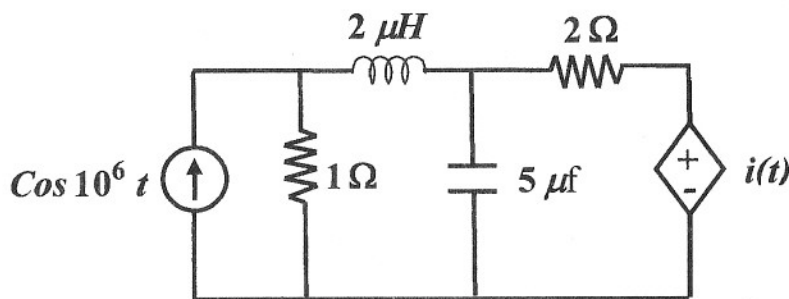


Figure 3A

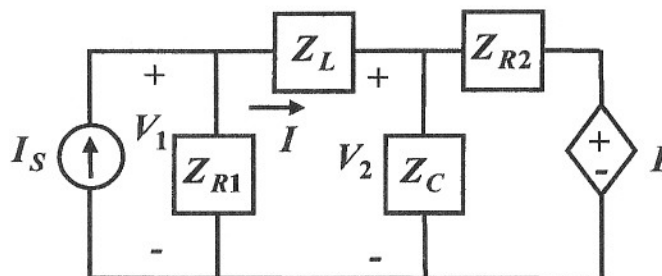


Figure 3B

國立清華大學命題紙

96 學年度 動力機械工程學系 乙 (電機控制) 組 碩士班入學考試

科目 電路學及電子學 科目代碼 1102 共 4 頁 第 3 頁 \*請在【答案卷內】內作答

4. The circuit shown in Fig. 4 is a general two-pole active filter formed by an ideal operational amplifier and four admittances  $Y_1$ ,  $Y_2$ ,  $Y_3$ , and  $Y_4$  of passive elements. Find the transfer function of  $V_o / V_i$  in terms of  $Y_1$ ,  $Y_2$ ,  $Y_3$ , and  $Y_4$ . (10%).

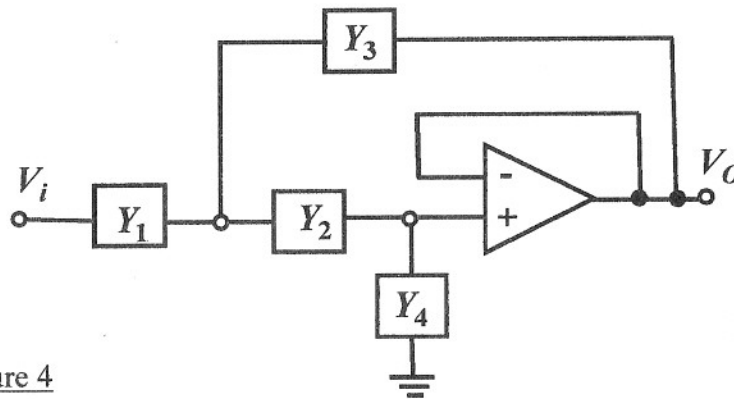


Figure 4

5. For the circuit shown in Fig. 5, the collector current of  $Q_2$  is  $I_{C2} = 1.6$  mA and the voltage across  $Q_2$  is  $V_{CE2} = 6$  V. Assume that  $\beta = 100$  and  $|V_{BE}| = 0.7$  V for the transistors.
- (a) Find  $R_{E2}$ . (5%)
- (b) Use the results of part (a) to find  $V_{EC1}$ . (5%)

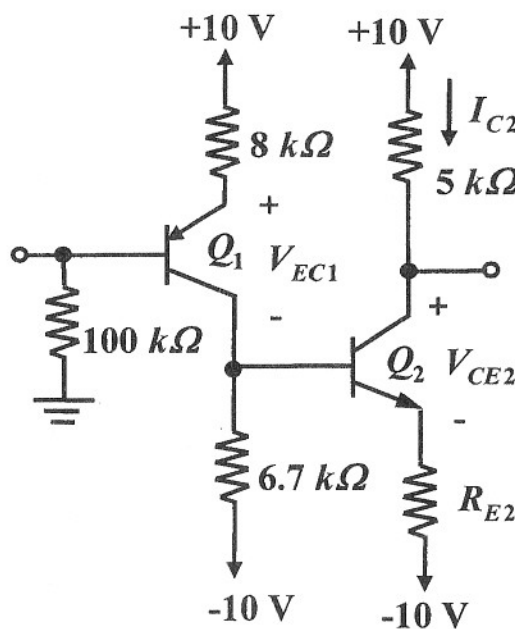


Figure 5

國立清華大學命題紙

96學年度 動力機機工程學系 乙(電機控制)組 碩士班入學考試

科目 電路學及電子學 科目代碼 1102 共 4 頁 第 4 頁 \*請在【答案卷內】內作答


6. The circuit shown in Fig. 6 is a MOSFET current mirror with active load.

(a) Draw the small-signal equivalent circuit. (5%)

(b) Derive the expression for the output resistance  $R_O$ . (5%)

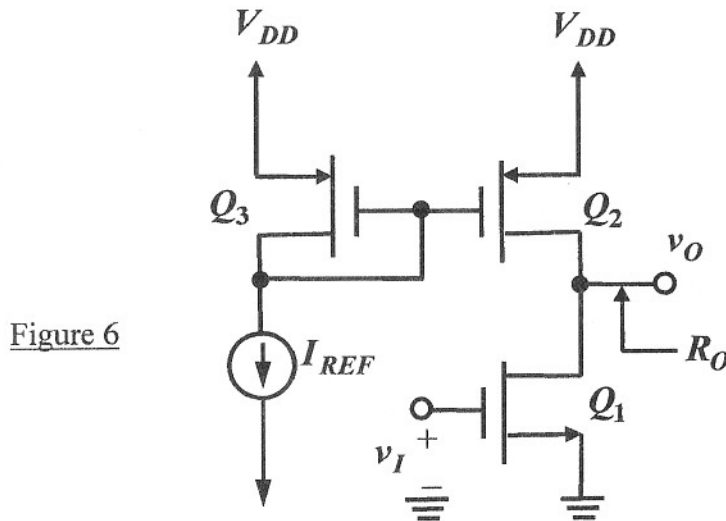(c) Derive the expression for the voltage gain  $v_O/v_I$ . (5%)

(Notice that please include the output resistance  $r_o$  of all transistors in your answers.)



7. The circuit shown in Fig. 7 is a common-gate amplifier with loads  $R_L$  and  $C_L$ . Using the open-circuit time constant method to estimate the 3-dB frequency  $f_H$  for the circuit. The body effect of the transistor can be neglected. In the transistor, only the internal capacitances between gate and drain  $C_{gd}$  and between gate and source  $C_{gs}$  are considered in this circuit. (15%)

