

1. (A) Explain why a typical magnitude response of an amplifier has a lower 3 dB and a upper 3 dB frequencies ? (5%)

(B) Let $V_{OH} = V_{DD}$, $V_{OL} = 0V$ for a digital inverter, find the average dynamic power of the gate with the load C_L only at the clock rate f . (5%)

2. For the circuit in Fig. P2, $\mu_n C_{ox} = 2.5 \mu_p C_{ox} = 20 \mu A/V^2$, $|V_e| = 1V$, $L = 10 \mu m$, Neglect the channel-length modulation effect. Find the labeled V and I , and show that the transistors are operating in the saturation region. (10%)

3. Find the output resistance R_o shown in Fig. P3. (10%)

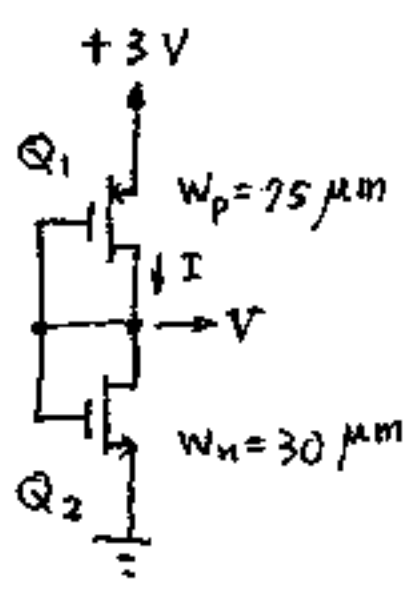


Fig. P2

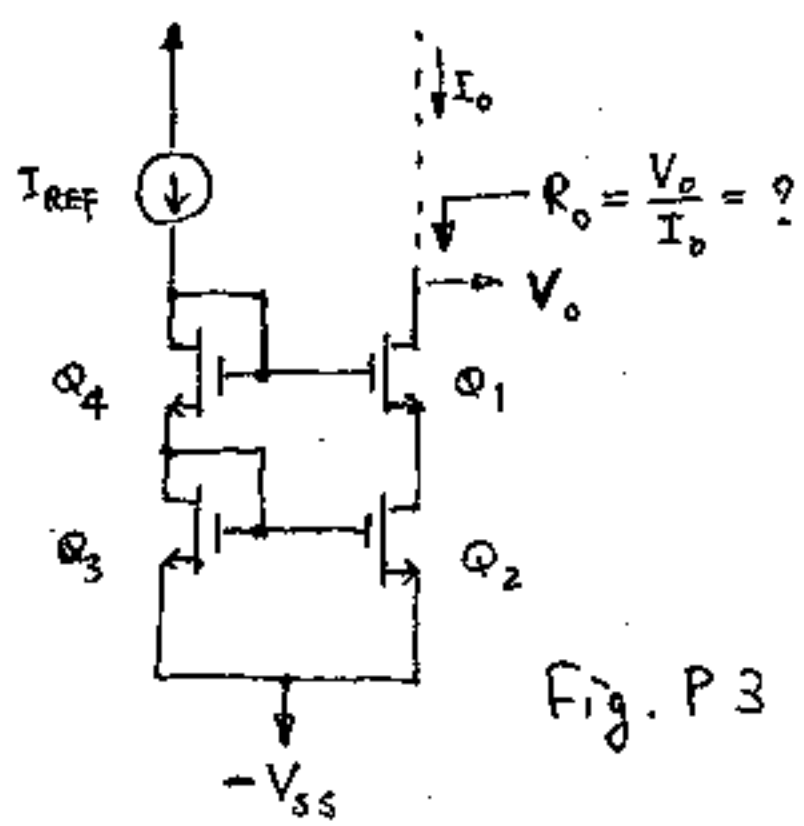


Fig. P3

4. For the amplifier shown in Fig. P4, find the voltage gain $A_v = \frac{v_o}{v_i} = ?$
(10%)

5. Use the approximate method based on the Miller effect to find the upper 3 dB frequency of the amplifier shown in Fig. P5, while

$k_n'(\frac{W}{L}) = 1 \text{ mA/V}^2$, and $C_{gs} = C_{gd} = 1 \text{ pF}$. (10%)

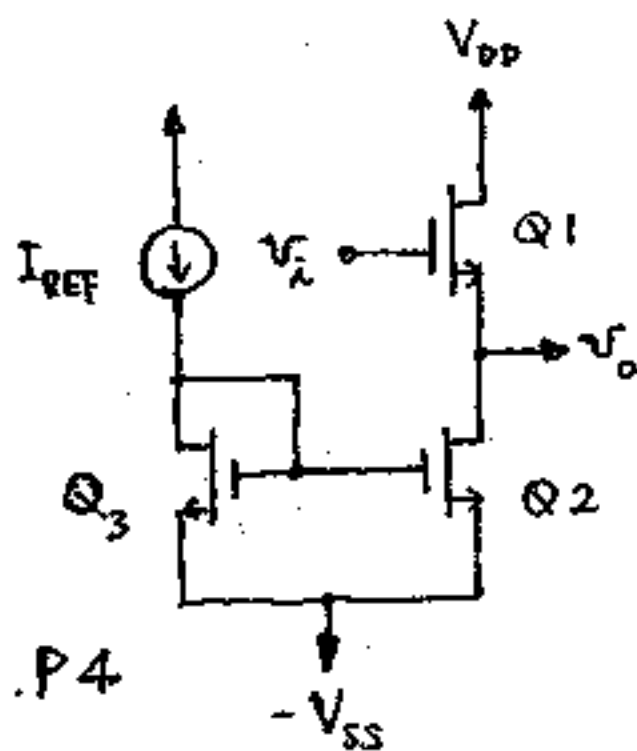


Fig. P4

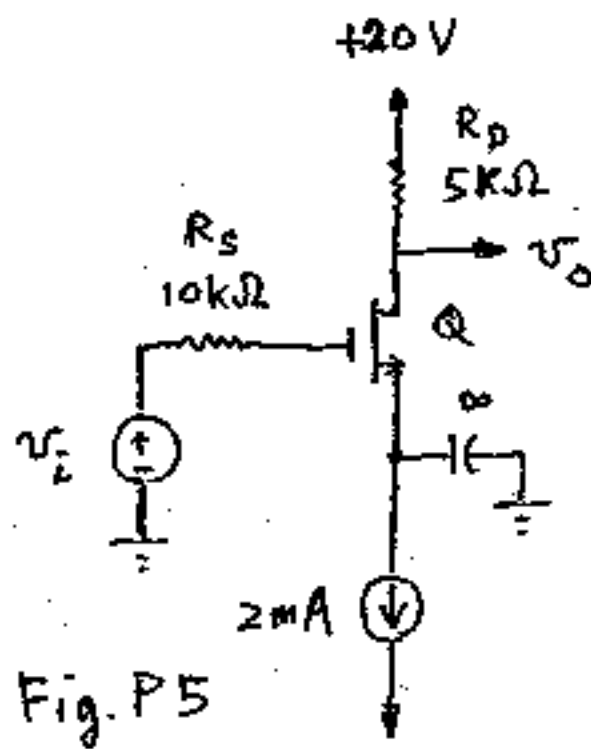


Fig. P5

----- Some useful formulas for NMOSFET -----

Saturation: $I_D = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$;

$$g_m = k_n' \left(\frac{W}{L}\right) (V_{GS} - V_t) = \left[2 k_n' \left(\frac{W}{L}\right) I_D \right]^{1/2}$$

$$r_o = V_A / I_D, \quad \lambda = 1 / V_A$$

Triode: $I_D = k_n' \left(\frac{W}{L}\right) \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$

6. For the circuit in Fig.P6, what feedback type it is ? For $R_{id}= 100\text{ k}\Omega$, $\mu= 10^4$, $r_o= 1\text{ k}\Omega$, $R_s= 10\text{ k}\Omega$, $R_L= 2\text{ k}\Omega$, find the close-loop gain A_f , input resistance R_{in} , and output resistance R_{out} . (16%)

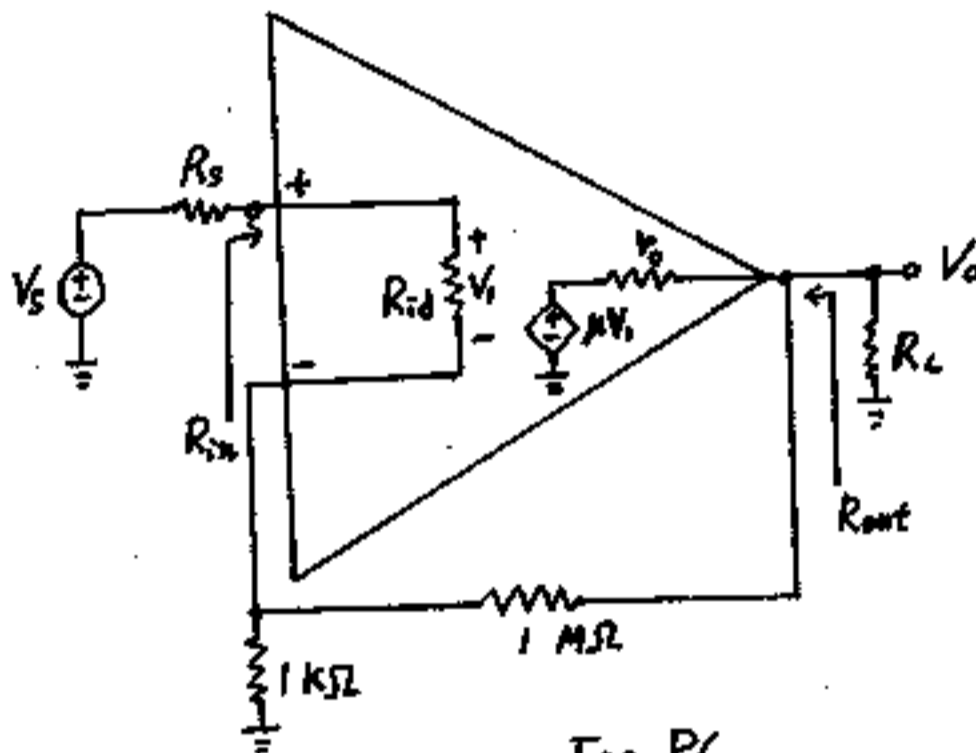


Fig. P6

7. For the circuit in Fig.P7, sketch the transfer curve (V_o vs V_i). (Remember to label some key values in the curve) (12%)

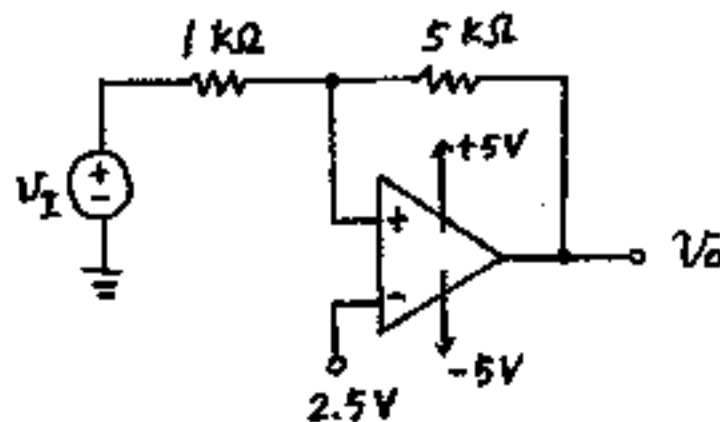


Fig. P7

8. A typical scheme of dual-slope analog-to-digital converter (ADC) is shown in Fig.P8. Identify the slopes S_1 and S_2 of V_1 to be fixed or variable. Also are the intervals of T_1 and T_2 fixed or variable? For the S_1 , S_2 , T_1 , and T_2 , which one (or ones) can be interpreted to the analog signal V_A ? (10%)


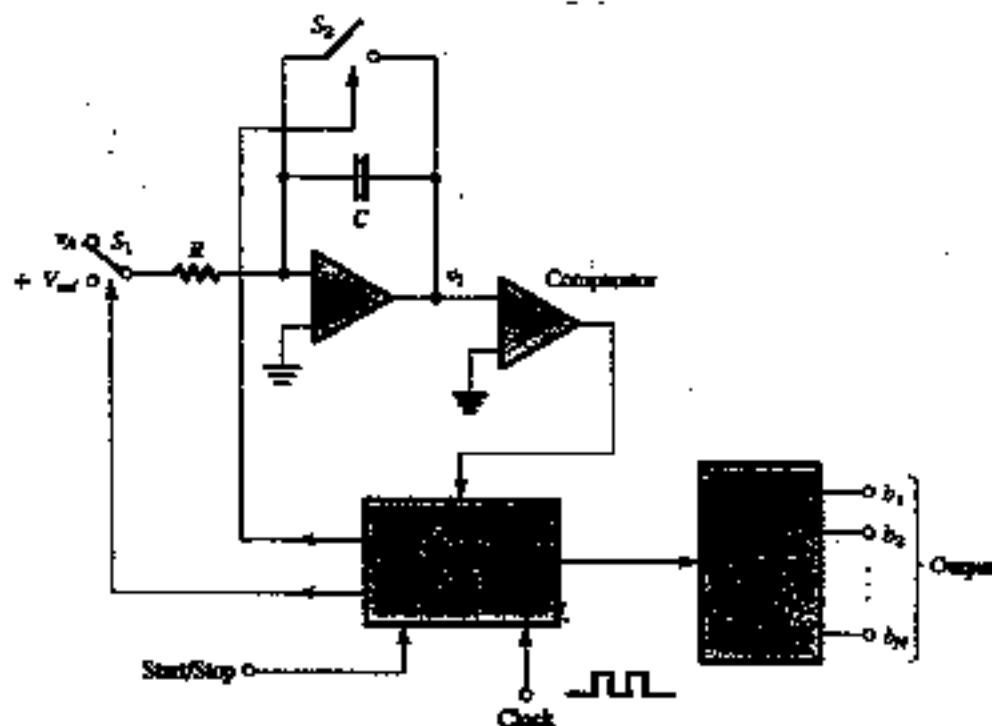


Fig. P8

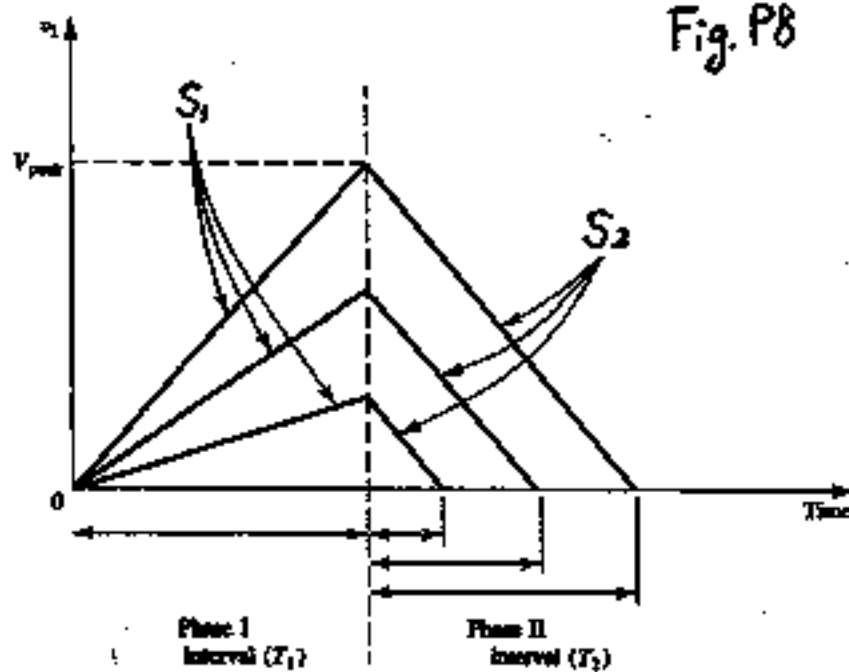

9. (a) Sketch the cross section figure of Erase-Programmable Read-Only-Memory (EPROM) (b) Sketch the transfer curves of it before and after data programming, then define the sense voltage point. (12%)