

1. In the differential amplifier circuit as shown, all transistors are matched with parameters $\beta=100$, $V_A=100$ V, $V_{BE(on)}=0.7$ V, $V_{CE,sat}=0.3$ V.

(1) Calculate the following parameters: (10%)

- g_m value of Q_1 and Q_2
- differential voltage gain $V_o/(V_1-V_2)$
- differential input resistance

(2) Find the minimum input common mode voltage $V_{CM,min}$ and the output voltage swing $V_{o,min}$, and $V_{o,max}$. (9%)

 


Fig. 1 for problem 1.

2. A common emitter amplifier was found to have a single-time-constant high frequency response with mid-band voltage gain of 40 dB and upper 3-dB frequency of 100 KHZ.

(1) Sketch the Bode plot for the voltage gain $|A|$ (3%)

(2) Find $|A|_{dB}$ for frequencies at 400 KHZ and 4 MHz. (5%)

3. In the circuit, the op-amp is ideal and the BJT has $\beta=\infty$.

(1) What is the feedback topology?

Explain your reason.

(2) Find the voltage gain V_o/V_s .

(3) Find the power dissipation on the BJT when $V_s=2$ V.

(8%)

 


Fig. 2 for problem 3.

科目：電子學 科號：4102/3802 共 3 頁第 2 頁 *請在試卷【答案卷】內作答

4. A lightly doped pn diode is used for light detector with $N_a=2 \times 10^{14} \text{ cm}^{-3}$ and $N_d=1 \times 10^{16} \text{ cm}^{-3}$. Assume the depletion region widths in the p region and the n region are W_p and W_n , respectively.
- What is W_p/W_n ? (5%)
 - Find the maximum W_p and W_n that can be obtained if the junction breaks down at reverse bias voltage of 30V and assume the critical field for junction breakdown is $1 \times 10^6 \text{ V/cm}$. (5%)
5. For a common-source stage with a resistor load is shown in Fig. 3 below. Assume $k_p=100 \mu\text{A/V}^2$, $W=20 \mu\text{m}$, $L=1 \mu\text{m}$, $V_T=1\text{V}$ and neglect channel length modulation effect for M1.
- Find the input bias range within which M1 is in saturation. (5%)
 - What is the maximum small-signal voltage gain of this circuit? (5%)
 - Propose changes in the circuit parameters so the input bias range can be increased. (5%)
 - Replace M1 with a BJT, Q1 with $I_s=1 \times 10^{-15} \text{ A}$ (neglect base current). Estimate the input bias range within which Q1 is in forward-active region. (5%) (FYI: $\ln 2=0.69$, $\ln 3=1.1$, $\ln 5=1.6$, $\ln 7=1.9$, $\ln 10=2.3$)

 


Fig.3 for problem 5.

6. For Fig. 4 below,

- (a) Draw the Input-output plot with explanations. 5%
 (b) What is this circuit's name? 5%
 (c) What are the limitations/constraints of this circuit? 5%

 


Fig. 4 for problem 6.

7. In Fig. 5, the saturated outputs for the ideal Op Amp are +10V and -10V,
 (a) If $V_{ref} = 0V$, draw the V_i - V_o plot with explanations. (5%)
 (b) If $V_{ref} = 5V$, draw the V_i - V_o plot with explanations. (5%)
 (c) How do you get precise output level by using a resistor and two Zener diodes? 5%
 (d) Also draw the V_i - V_o plot in (c) and show the values of the output levels with $V_{Z,reverse} = 5V$ and $V_{Z,forward} = 0.5V$ (5%)

 


Fig. 5 for problem 7