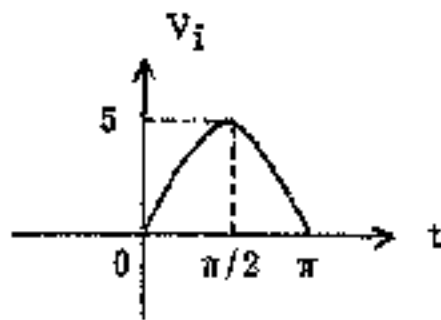


國立清華大學命題紙


八十四學年度 電機 所 甲 組碩士班研究生入學考試

科目 電路學 科號 2202 共 2 頁第 1 頁 *請在試卷【答案卷】內作答

1. The sinusoidal voltage pulse below in (a) is applied to the circuit shown in (b). Use the convolution integral to find the value of V_0 at $t = \frac{\pi}{4}$ sec. (15%)




(a)

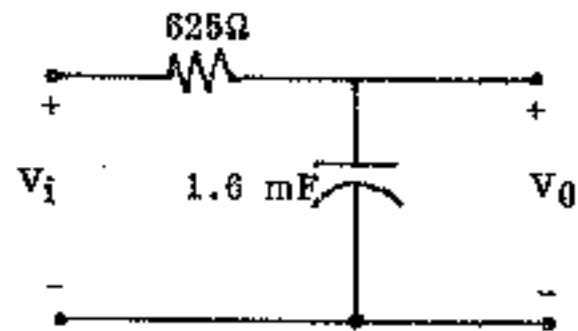

(b)

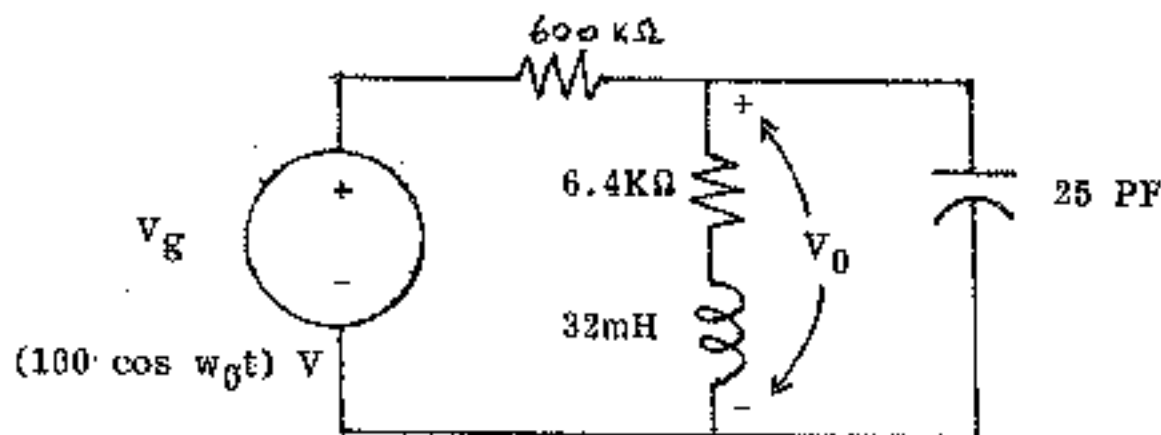2. The frequency of the sinusoidal voltage source in the circuit below is adjusted to unity power-factor resonance. (15%)
- (a) What is the Q of the coil at the resonant frequency?
- (b) What is the peak amplitude of V_0 at resonant frequency?




3. The impedance of a series RLC circuit is $400 + j 3800 \Omega$ at a frequency of 20 K rad/s . The circuit is scaled in magnitude and frequency by the same factor, and when the impedance is measured at 5 K rad/s , it is found to be $1600 - j 11,800 \Omega$.
- (a) Calculate the original values of R , L , and C .
- (b) Calculate the resonant frequency. (15%)


八十四學年度 電機 所 甲 組碩士班研究生入學考試

科目 電路學 科號 2202 共 2 頁第 2 頁 *請在試卷【答案卷】內作答

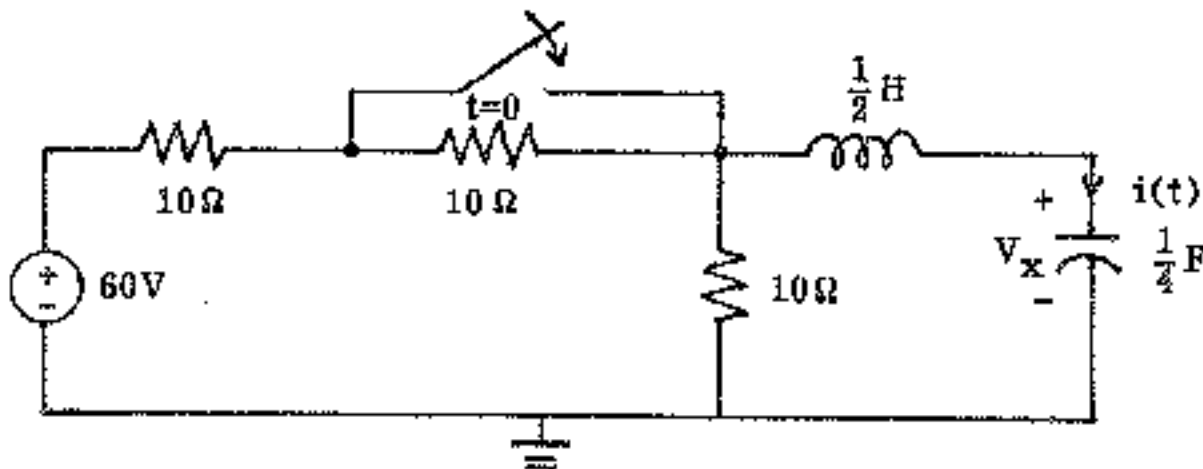4. For the following network, the switch has been open for a very long time and is closed at $t=0$. Please find $i(t)$ for $t>0$. (20%)



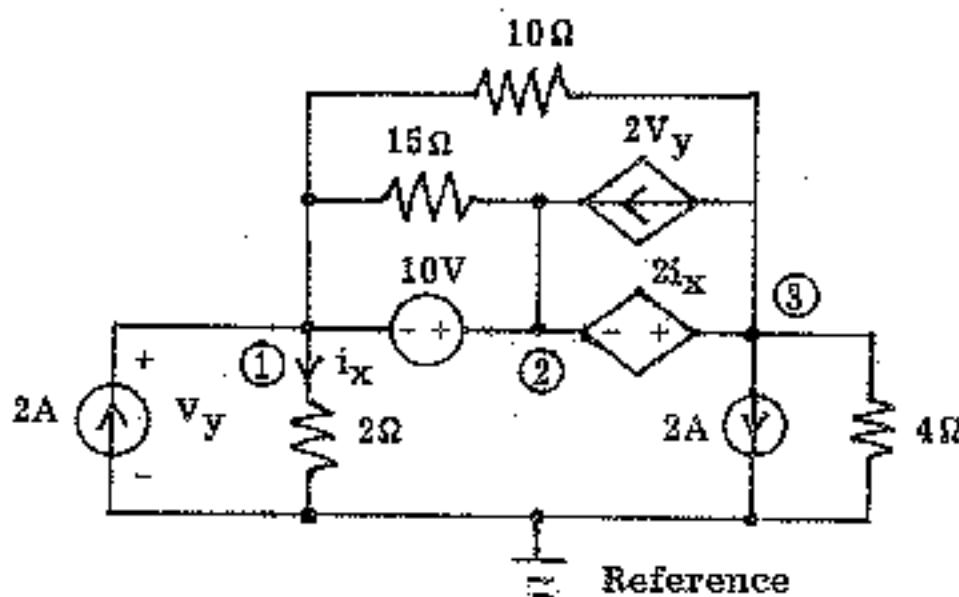5. Find the voltages at different nodes (i.e., V_1 , V_2 , V_3) for the following network. (15%)



6. In the following three phase system, it is assumed the wattmeter is ideal and the balanced Y-connected load is connected to a balanced three phase voltage source. If the load consumes complex power $S = 1000\sqrt{3} \angle 30^\circ$ VA, find the reading of the wattmeter. (20%)

