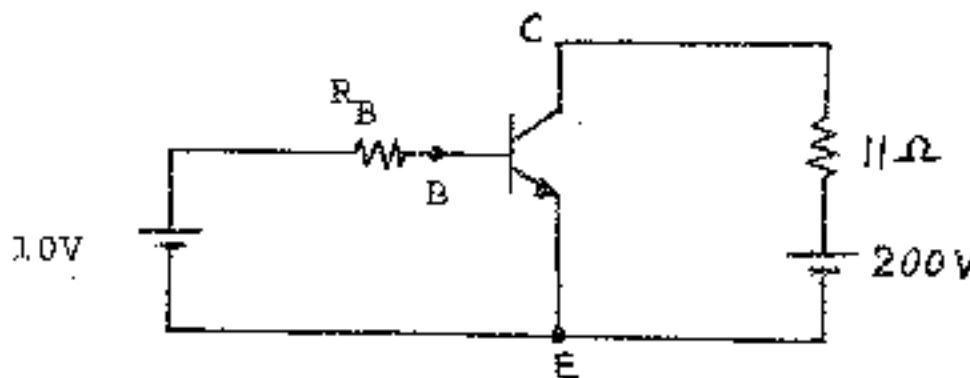



國立清華大學命題紙

八十四學年度 電機 所 甲 組碩士班研究生入學考試
 科目 電力電子 科號 2204 共 2 頁第 1 頁 *請在試卷【答案卷】內作答

1. In the following circuit, the bipolar transistor has the parameters of $V_{CE(sat)}=1.0V$, $V_{BE(sat)}=1.5V$ and $\beta=8$, find
 (a) the value of R_B to result in saturation with an overdrive factor of 5; (b) the forced β_f . (15%)



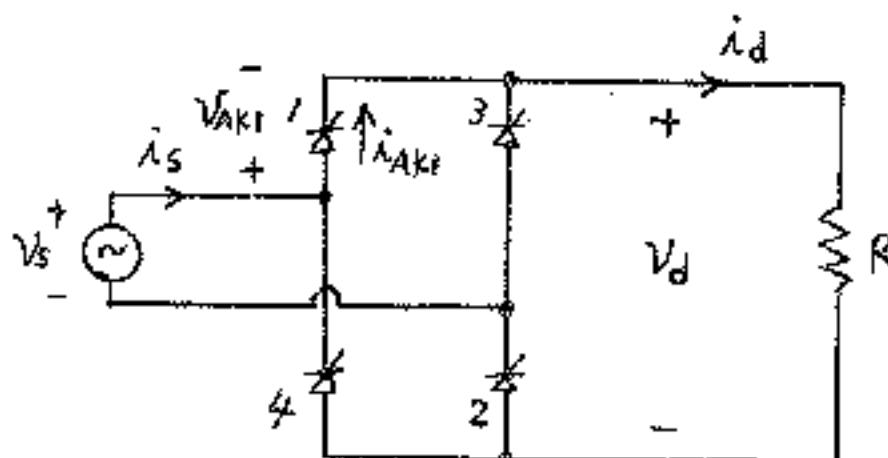2. (a) Draw the switching model of MOSFETs.
 (b) Draw a typical switching waveform and define the turn-on delay time, rise time, turn-off delay time and the fall time. (15%)
3. What are the advantages and disadvantages of using (a) pulse transformers (b) optocouplers for floating or isolating the gate signals of transistors with respect to ground? (15%)
4. In the following converter circuit, $v_s = \sqrt{2}V_s \sin \omega t$ and the triggering angle $\alpha = 90^\circ$:
 (1) Sketch the waveforms of v_s , i_s , v_d , i_d , v_{AK1} and i_{AK1} .
 (2) Determine (a) average value of v_d ; (b) average value of i_{AK1} ; (c) rms value of i_{AK1} ; and (d) input power factor. (20%)




5. Explain the following terms:
 (1) Foldback current limiting; (2) Blanking time; (3) ESR;
 (4) Current-mode control. (10%)


國立清華大學命題紙

八十四學年度 電機 所 甲 組碩士班研究生入學考試
 科目 電力電子 科號 2204 共 2 頁第 2 頁 *請在試卷【答案卷】內作答

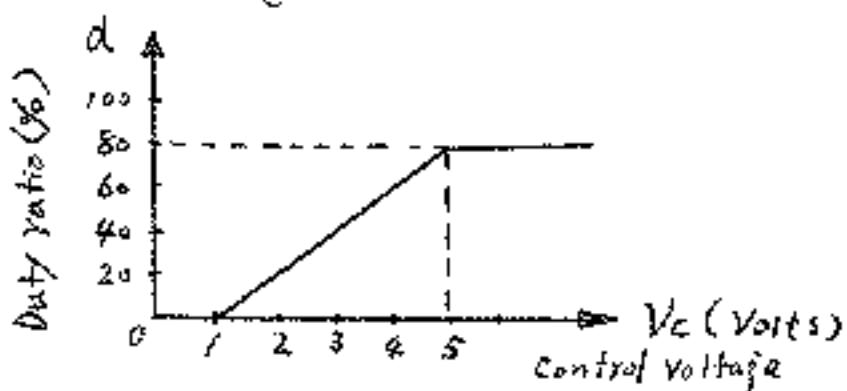6. (1) If the transfer characteristic between the duty-ratio d and the control voltage v_c is as shown, find the transfer function of $\tilde{d}(s)/\tilde{v}_c(s)$.
 (10%)



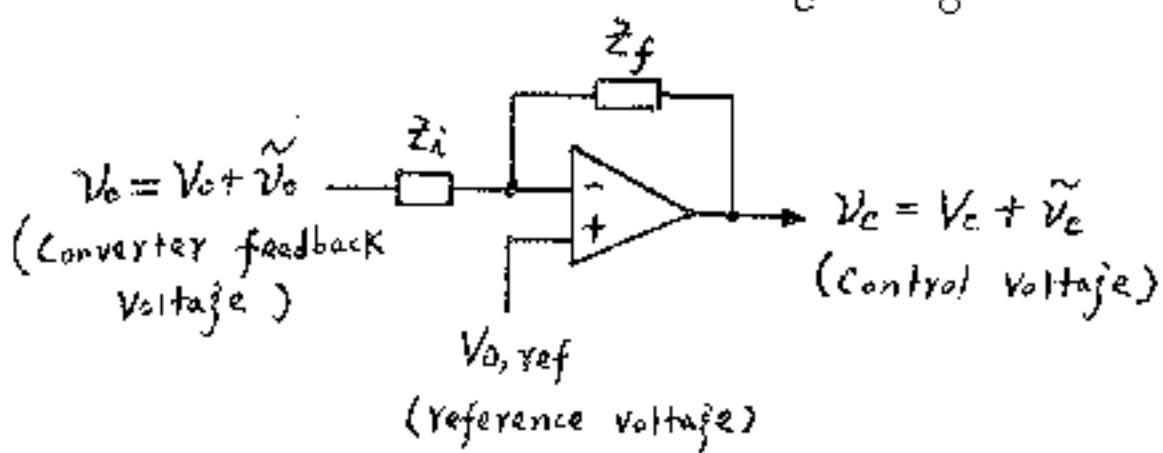- (2) For the compensated error amplifier circuit as shown, find the transfer function $\tilde{v}_c(s)/\tilde{v}_o(s)$.



7. For the three-phase bridge inverter with its gating signals as shown, draw the following waveforms: (1) v_{ab}, v_{bc}, v_{ca} and (2) v_{an}, v_{bn}, v_{cn} . (15%)

