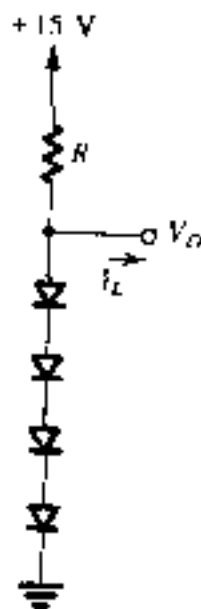



八十七學年度 電機工程系(陸) 丙 組碩士班研究生入學考試

科目 電子學 科號 3103 共 3 頁第 1 頁 *請在試卷【答案卷】內作答

1. Design the following circuit so that $V_o = 3V$ when $I_L = 0$, and V_o changes by 40mV per 1mA of load current. Find the value of R and the junction area of each diode (assume all four diodes are equal) relative to a diode with 0.7V drop at 1mA current. Assume $n=1$. (15%)



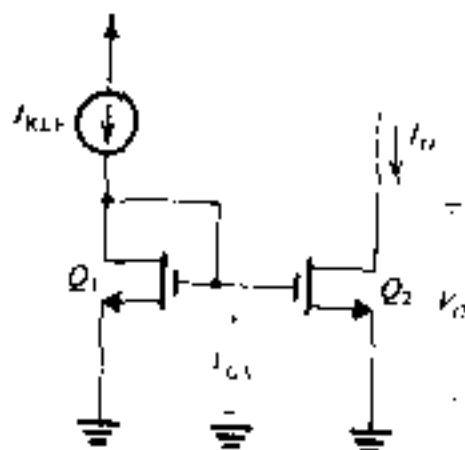2. The current mirror circuit has $L_1=L_2=6\mu m$, $V_1=1V$, $\mu_n C_{ox}=20\mu A/V^2$, $V_A=50V$, and $I_{REF}=10\mu A$. (a) Calculate the value of V_{GS} . (b) Find the value of W_2 that will result in an output current of $100\mu A$ when the output voltage is equal to the voltage at the gate. (c) If the output voltage increases by 5V, find the resulting value of I_o . (15%)



3. A differential amplifier as shown in Figure A has an ideal current source I with infinite internal resistance. Apply a small signal v_d to the differential input terminals, derive the expressions for
- the small signal transconductance of the transistor g_m
 - the small signal emitter current i_e
 - the input differential resistance R_{id}
 - the differential voltage gain when the output is taken differentially A_d (20%)

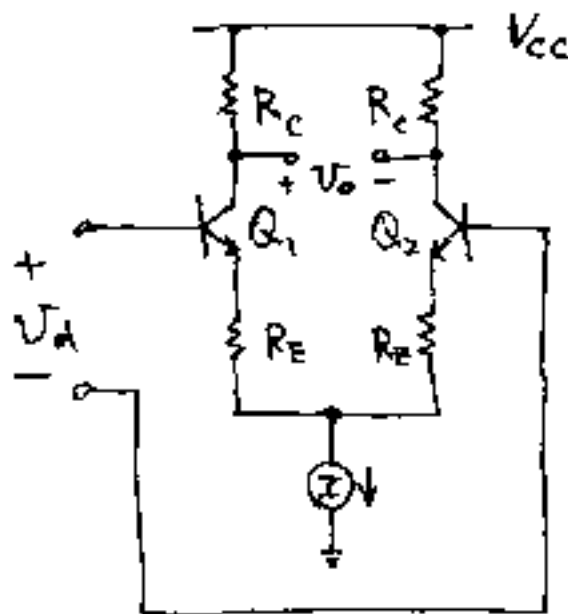


Figure A

4. A output stage amplifier as shown in figure C.
- Is this a class A, B, or C amplifier?
 - What is the main problem of this class of amplifier as far as signal quality is concerned?
 - Propose a modified circuit to eliminate the problem you stated in part (b). (15%)


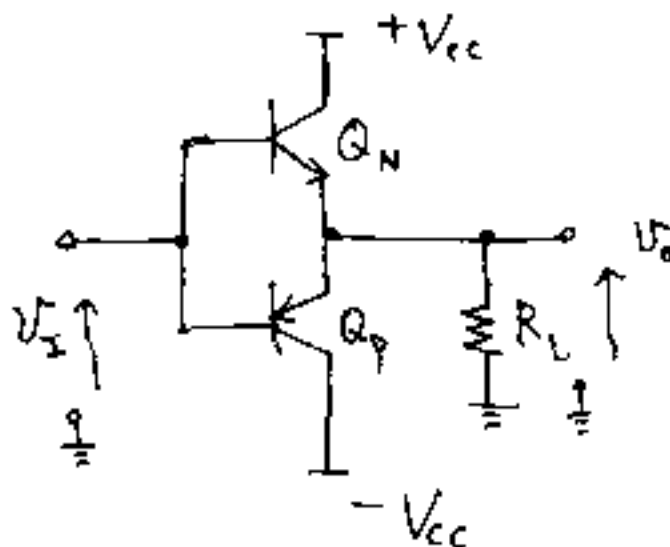



Figure C

5. Give the transfer function of a second order bandpass filter with a center frequency of 10^3 rad/s, a center frequency gain of 10, and a 3-dB bandwidth of 10^3 rad/s (10%)

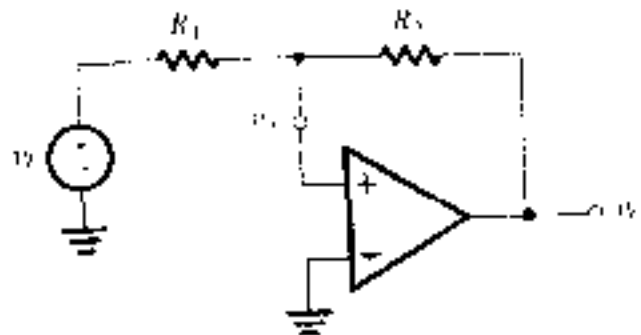6. The circuit has $\pm 10V$ output saturation levels and $R_1=1k\Omega$. Find a value for R that gives hysteresis of 100mV width. (10%)



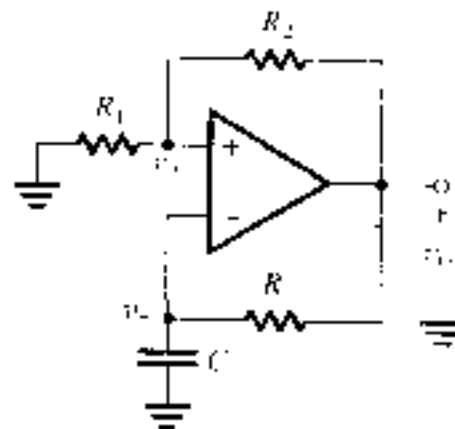7. For the circuit shown below, let the op amp saturation voltages be $\pm 10V$, $R_1=100k\Omega$, $R_2=R=1M\Omega$, and $C=0.01 \mu F$. Find the frequency of oscillation. (15%)



Natural logarithm $e = 2.718$

$\ln 2=0.6931$, $\ln 3=1.0986$, $\ln 5=1.6094$