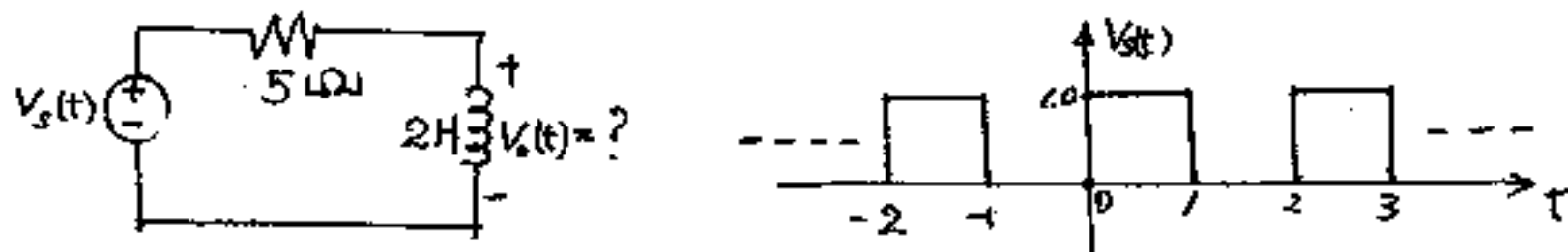


1. Let the voltage source $V_s(t)$ be given as below,

- (a) Find the Fourier series of the voltage source. (10%)
 (b) Find the first three sinusoidal terms of the output voltage $V_o(t)$. (10%)

You don't need to calculate the values of $\sqrt{(\cdot)}$ and $\tan^{-1}(\cdot)$ in the answer.




2.(a) Find the Thevenin's equivalent circuit as seen from terminals a-b.

Please use amplitude voltage phasor and impedance! (15%)

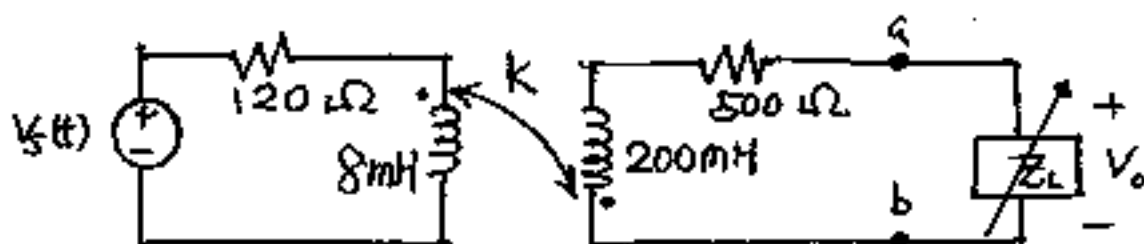(c) Find the load impedance Z_L for maximum output power. (5%)

The coefficient of coupling of the mutual inductors k is equal to 0.8 and the input voltage source is $V_s(t) = 125 \cos 5000t$ V.



3. Calculate the reading of each wattmeter in the following circuit. (10%)

The three-phase voltage is given as

$$V_a(t) = 120\sqrt{2} \cos \omega t \text{ V}$$

$$V_b(t) = 120\sqrt{2} \cos (\omega t - 120^\circ) \text{ V}$$

$$V_c(t) = 120\sqrt{2} \cos (\omega t + 120^\circ) \text{ V}$$


$$Z = 10 \angle -75^\circ \Omega$$

$$\sin 15^\circ = \cos 75^\circ = 0.2588$$


$$\sin 45^\circ = \cos 45^\circ = 0.707$$

$$\sin 30^\circ = 0.500$$

$$\cos 30^\circ = 0.866$$

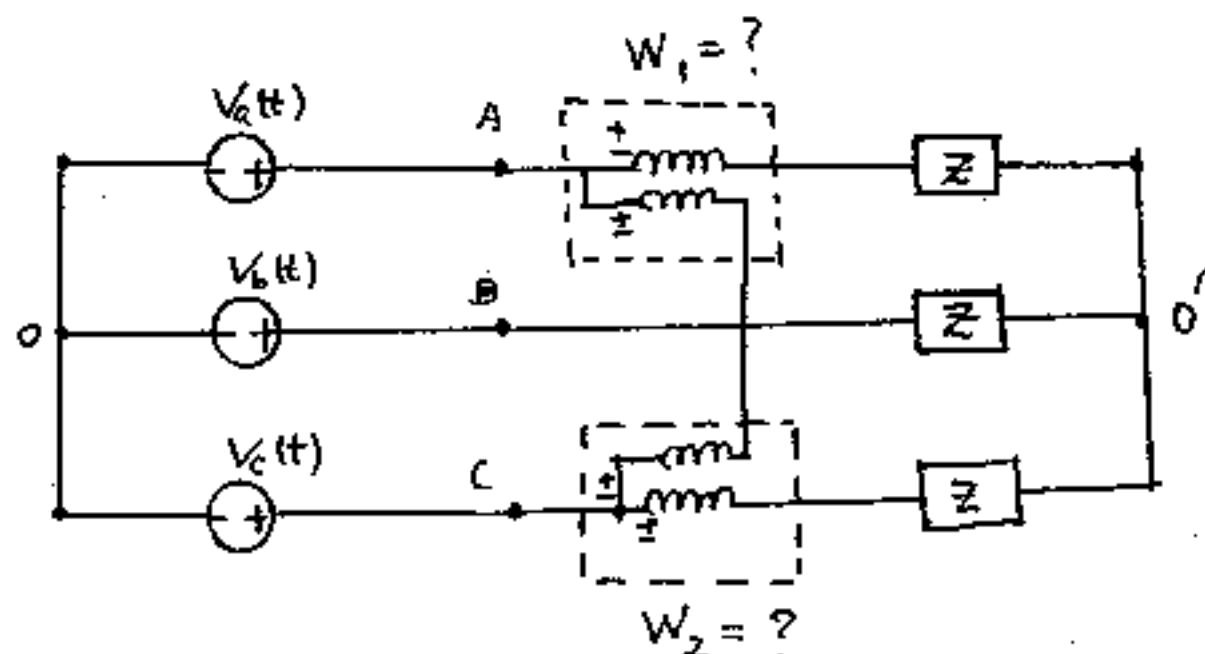


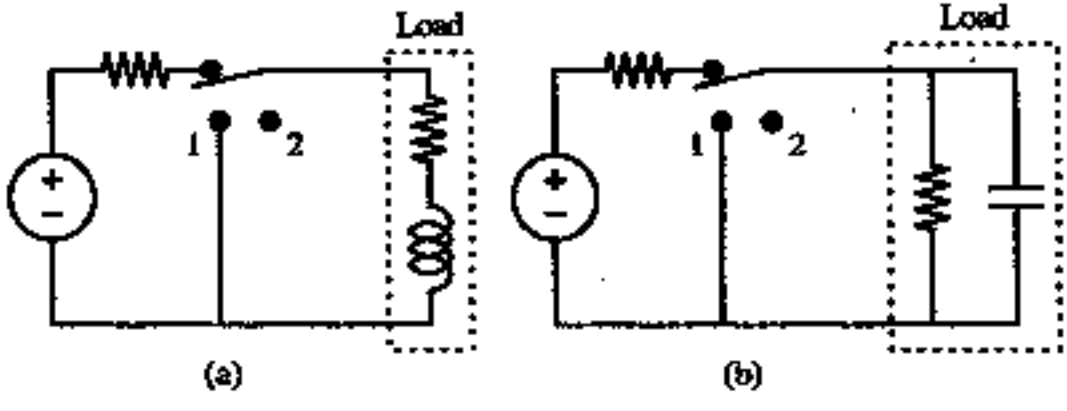4. For the following circuits, which switch position would you choose to shut down the load? Explain your answer.




10%

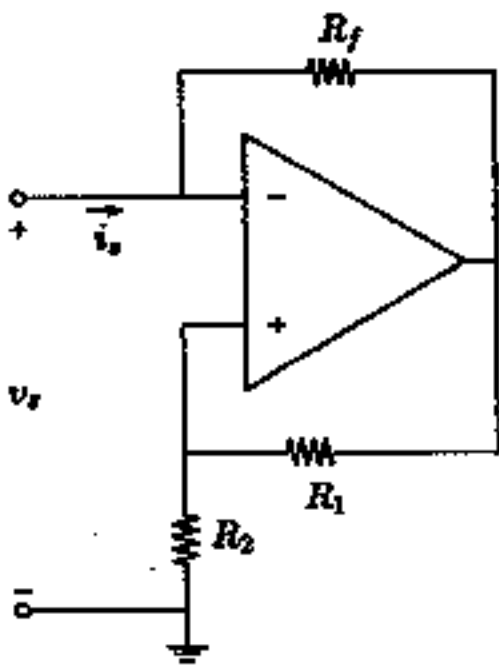5. Assume the ideal OPAMP is powered by $+V_{cc}$ and $-V_{cc}$. Find the relationship between v_o and i_o in (1) linear operation; (2) positive saturation; (3) negative saturation.



20%

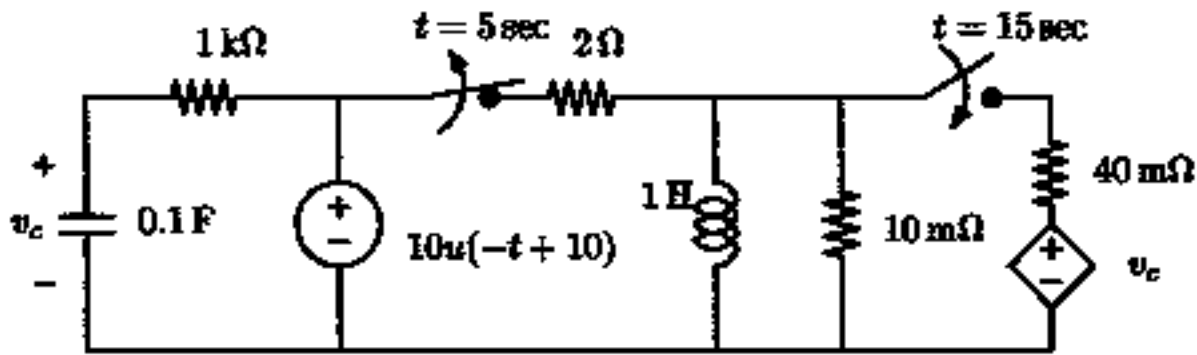6. Find $i_L(t)$ in the given circuit below. $u(t)$: step function. ($e^{-0.1} = 0.9; e^{-0.05} = 0.95; e^{-0.01} = 0.99$)



20%