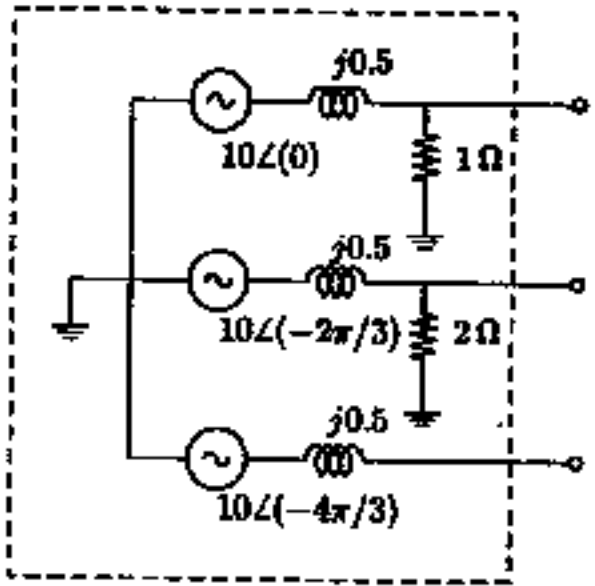



**Circuit Analysis**

1. Find the Thevenin's equivalent of the given circuit. (10%)



**Per Unit**

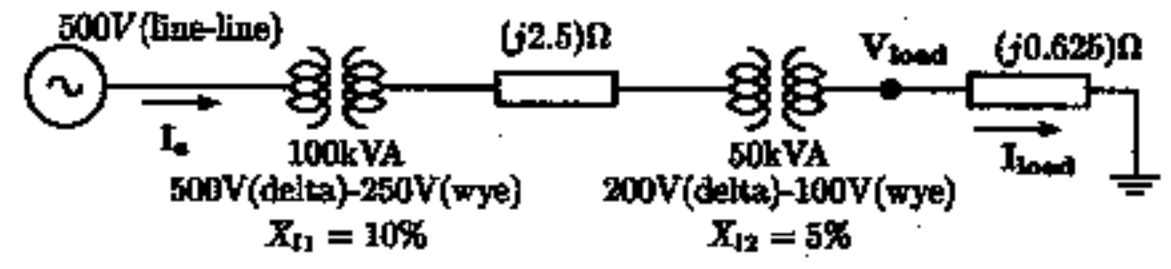
2. Refer to the one-line diagram of a fictitious power system below. Calculate the following based on the name-plate values of the transformers (reactances given in percent), line impedance (in Ω) and load impedance (in Ω): (1) load voltage  $V_{load}$ ; (2) source current  $I_s$ . Assume the generator and load are both Y-connected.  
 Note  $\frac{1}{\sqrt{3}} = 0.577$ . (15%)



**Transient Analysis**

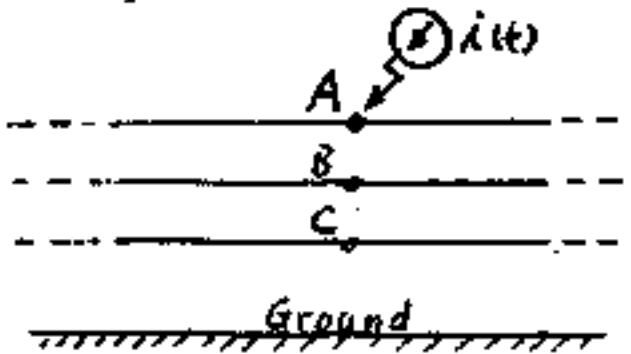3. A lightning current stroke to phase A of a three-phase line as shown. The line surge impedance matrix is

$$R = \begin{bmatrix} 500 & 50 & 25 \\ 50 & 500 & 50 \\ 25 & 50 & 500 \end{bmatrix} \Omega$$




(a) Find the voltage build-up at points A, B and C over a time span during which

reflections have not yet come back from the remote ends of the line.

- (b) Suppose that  $v_B = k_1 v_A$  and  $v_C = k_2 v_A$ ;  $k_1$  and  $k_2$  are proportional constants. Find  $k_1 = ?$ ,  $k_2 = ?$  (15%)

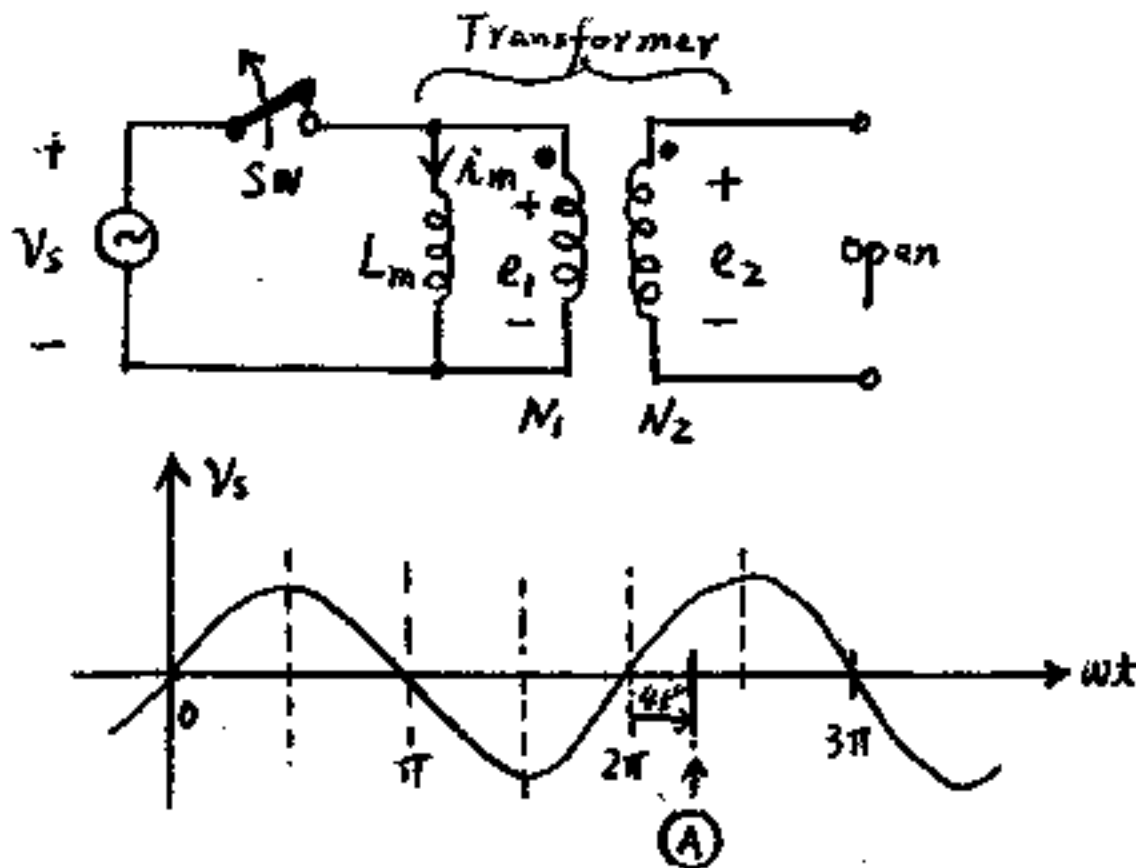4. The switch SW is originally closed steadily, and it is opened at the time instant denoted by (A). Sketch the following waveforms:  $e_1$ ,  $i_m$ , and  $e_2$ . (10%)




### Power Flow

5. For the power system shown below, the system bus admittance is

$$Y_{bus} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

where  $y_{21} = 1.9 \angle \theta_1$  and  $y_{22} = 1.8 \angle \theta_2$ . Assume:

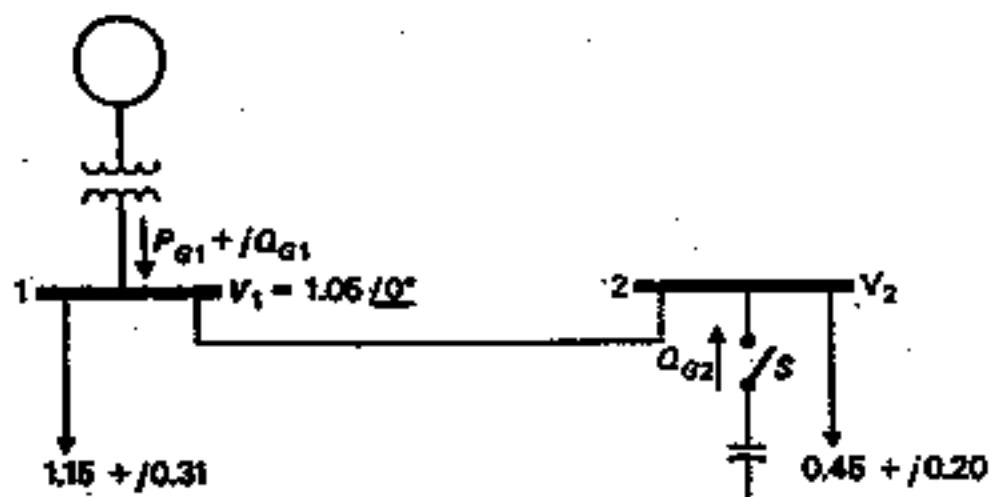- The switched capacitor at bus 2 is out;
- The power bases selected are  $S_b = 300 \text{ MVA}$ ,  $V_b = 230 \text{ kV}$ ;
- The line reactance between buses 1 and 2 is  $91 \Omega$ .



Answer the following questions:

(a) Estimate  $\theta_1$  and  $\theta_2$  by selecting one of the following combinations:

$$\theta_1 = 99^\circ, \theta_2 = -80^\circ$$

$$\theta_1 = -99^\circ, \theta_2 = 80^\circ$$

$$\theta_1 = 9^\circ, \theta_2 = -10^\circ$$

$$\theta_1 = -9^\circ, \theta_2 = 10^\circ$$

(b) Let  $V_2^{(0)}$  denote the initial guess of bus 2 voltage. Which do you give among the following to  $|V_2^{(0)}|$ ?

$$0.95 \text{ pu kV}$$

$$1.00 \text{ pu kV}$$

$$1.05 \text{ pu kV}$$

Select one of them.

(c) Let  $\delta^{(0)}$  denote the phasor angle for  $V_2^{(0)}$ . Write down your formula to estimate  $\delta^{(0)}$  (You are not requested to actually calculate  $\delta^{(0)}$ ).

(d) Having obtained  $|V_2^{(0)}| \angle \delta^{(0)}$ , write down the Gauss-Seidel iterative computation formula to calculate  $V_2^{(1)} = |V_2^{(1)}| \angle \delta^{(1)}$  (Assume  $\delta^{(0)} = 13.5^\circ$ . Also, you are not requested to actually calculate  $V_2^{(1)}$ ).

(e) Now we energize the capacitor at bus 2, and give an initial guess for  $V_2$  at  $V_2^{(0)} = 1.0 \angle -10^\circ$ . Rewrite the Gauss-Seidel iterative computation formula to calculate  $V_2^{(1)} = |V_2^{(1)}| \angle \delta^{(1)}$ . (Note: In this case, you can not actually calculate  $V_2^{(1)}$ , because you have not estimated the reactive power injection into bus 2, i.e., you have not estimated  $Q_2^{(0)} = Q_{G2}^{(0)} - 0.20$ ).

(f) After the energization of capacitor at bus 2, which can you observe in the system?

(1) Line loss decreases.

(2) Line charge increases.

(3)  $P_{G1}$  decreases.

(4)  $\delta_2$  decreases.

(5) None is correct.

Give you selections (You are allowed to give multiple selections. If any one selection is incorrect, Problem (f) will not be given any credit). (25%)

**Fault Analysis**

6. For the generator in Problem 1. Let  $E_a$ ,  $E_b$  and  $E_c$  denote:

$$E_a = 10 \angle 0$$
$$E_b = 10 \angle -2\pi/3$$
$$E_c = 10 \angle -4\pi/3$$

Assume a direct ground fault occurs at the generator terminal of phase a. Can you compute the fault current by using sequence network? If your answer is positive, draw the sequence network; otherwise, give your explanation. (10%)

**Protection**

7. Answer yes or no, and give your brief explanation (give key phrases only, not more than 10 Chinese characters for each answer).

- (a) Stator voltage unbalance can cause stator overheating on the winding but not on the iron.
- (b) Generator's loss of excitation can cause overheating of stator winding and stator end core.
- (c) Assume fuse A is closer to the power source than fuse B. To coordinate these two fuses. The minimum clearing time (MinCT) of fuse A is longer than the Maximum melting time (MaxMT) of fuse B. (15%)