

Power Quality

1. Three identical single-phase nonlinear loads are placed on the secondary side of a three-phase four-wire, Y-connected system as shown. If the load voltage and current of phase a are:
- (15%)


$$V_m = 120\sqrt{2} \sin 2\pi 60t \dots\dots\dots (V)$$

$$i_a = 50\sqrt{2} \sin(2\pi 60t - 30^\circ) + 40\sqrt{2} \sin(2\pi 180t - 40^\circ) +$$

$$\dots\dots 30\sqrt{2} \sin(2\pi 300t - 50^\circ) + 20\sqrt{2} \sin(2\pi 420t - 60^\circ) +$$

$$\dots\dots 10\sqrt{2} \sin(2\pi 540t - 70^\circ) \dots\dots (A)$$

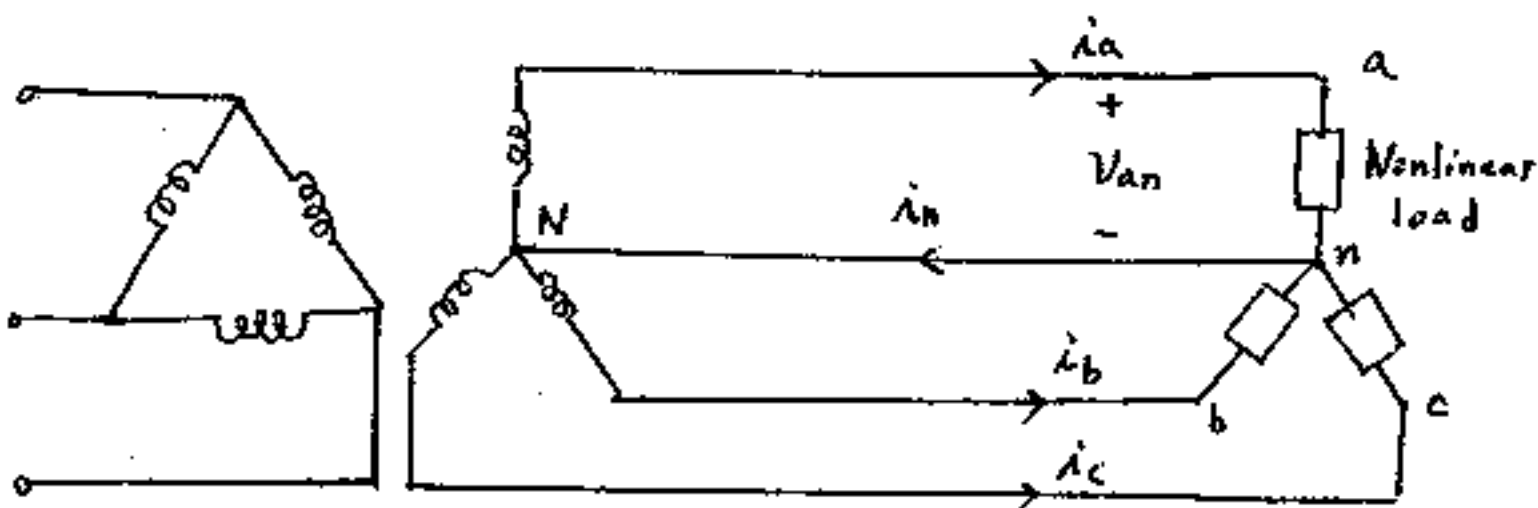- (1) Calculate the rms currents in each phase conductor and in the neutral conductor.
- (2) Calculate the average three-phase load power.



Dynamics


2. (1) The reservoir of a pumped-storage facility is separated by 400m in altitude, and it is 1.0km square and 5.0m deep. Find its stored energy.
- (2) Assuming the generation process is 80% efficient, how long would the stored water operate the six 400,000kva generators? Assume they are operated at the rated load with unity power factor.

(Note: $1.0 m^3$ of water has a mass of 1000kg, gravitational acceleration $g=9.81 m/s^2$, $1.0kwh=3.6MJ$)

(10%)

Per Unit

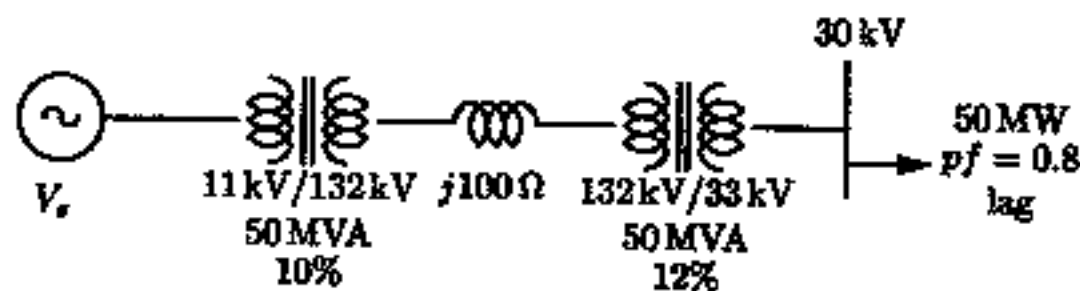
3. For the given transmission system, the load draws 50MW at $pf=0.8(\text{lag})$ from the voltage bus which is maintained at 30kV. Find V_s in volt. (15%)



Circuit Theory

4. A synchronous generator, modeled by a voltage source with an inductive reactance X_1 , connected in series, is connected to a load consisting of inductive reactance X_2 and a variable resistor R in parallel. Find R (in terms of X_1 and X_2) so that the output power of the generator is maximum. (10%)

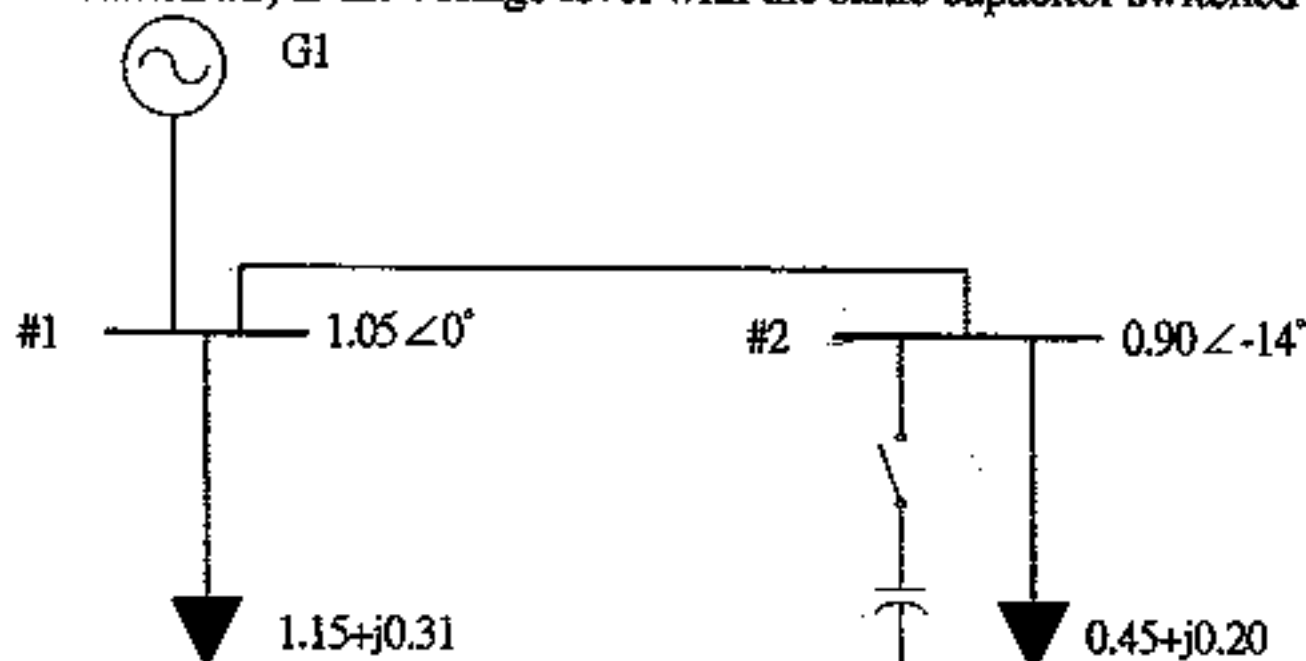5. For an artificial power system below. Assume the line between substation #1 and #2 is a medium-distance line. The figure, 0.90 P.U., for bus #2 (or substation #2) is the voltage level with the static capacitor switched off. (15%)



- (1) Compare the power flow results before and after the static capacitor switched on. That is, indicate how the following will be changed after the static capacitor switched on.
- The reactive power output for generator G1.
 - Line loss.
 - Line charge.
 - Voltage magnitude for bus 2.
 - Voltage angle for bus 2.

(2) Simulate the above power flow problem by the Newton-Raphson (N-R) method. In the N-R model formulation, let $m \times n$ represent the dimension of Jacobian matrix. Give $m \times n$ in the following conditions:

- With the static capacitor off.
- With the static capacitor on.

Fault Analysis and Protection

6. For an industrial power system, assume a phase-A-to ground fault occurs at the system main bus as shown below. (25%)

(a) Draw the sequence diagram for this faulted power system. In that diagram, indicate:

- the system reactance of Taipower (or the system reactance at duty point), X_{S1} , X_{S2} , X_{S0} ;
- the leakage reactance of 11.4kV main transformer (X_{t1} , X_{t2} , X_{t0});
- the reactance of induction motor (X_{m1} , X_{m2} , X_{m0}).


(b) Compare the relative magnitude among X_{m1} , X_{m2} , X_{m0} . Also give reasons for your comparison results.

(c) Write a formula to calculate the fault current I_f in terms of the above system parameters.

(d) Explain how X_{S1} is derived. Give the derivation procedure.

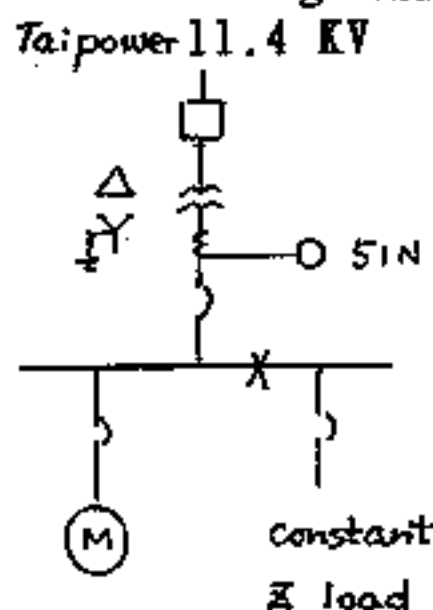(e) Draw the CT connection for 51N.

In your drawing, indicate how the ground fault can be detected.



Stability

7. Power system transmission system (T/S) requires high-speed protection, mainly to meet the critical clearing time (CCT) requirement. In contrast, the distribution system (D/S) does not have such requirement. (10%)

(a) Define CCT.

(b) Why does T/S have CCT requirement, but not D/S?