

1. The diodes in the circuit are ideal. The resistors are  $R_1=R_2=R_3$ . The voltage  $V_1=10$  V. Determine the voltage  $V_o$  for  $V_2=(a) 10$  V, (b) 2 V, (c) -1 V, (d) -10 V and (e) -13 V.

(10% Fig. P1)

 


Fig. P1

2. In the voltage regulator as shown, the parameters are  $V_{z0}=5.7$  V,  $r_z=10$   $\Omega$  for the zener diode and  $\beta=100$  for the BJT, and  $R_1=R_2=1$  k $\Omega$ . The supply voltage is  $V_{PS}=10$  V  $\pm 10\%$ . The output voltage is  $V_o=5$  V  $\pm \Delta\%$ . Find the value of  $\Delta$  and the output resistance  $R_{out}$ .

(10% Fig. P2)

 


Fig. P2

3. The transistor parameters in the circuit are  $\beta=100$ ,  $V_A=100$  V for the BJT;  $K_n=1$  mA/V<sup>2</sup>,  $\lambda=0.02$  V<sup>-1</sup> for the FET. The capacitor  $C=\infty$ . The voltage  $V_S$  and the resistors  $R_1$ ,  $R_2$ ,  $R_3$  are designed such that the collector and drain currents are  $I_{CQ}=I_{DQ}=1$  mA. Determine the voltage gain  $V_o/V_i$  and the output resistance  $R_{out}$ .

(15% Fig. P3)

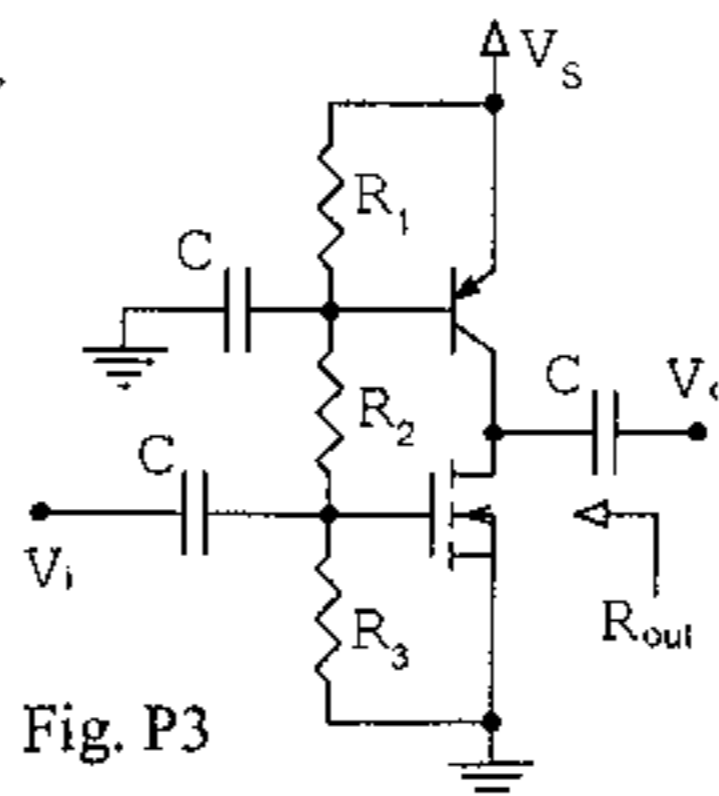


Fig. P3

4. For a single common source device, please derive its unity-current-gain frequency. (draw the small signal model and consider all the parasitic capacitances and output resistance). (10%)
5. Fig. P5 is a differential amplifier with  $I_{D5}=0.2\text{mA}$ . If all the devices are biased with  $V_{GS}-V_t = 0.2\text{V}$ , where NMOS and PMOS threshold voltages are  $V_{tn}=|V_{tp}|=0.6\text{V}$ . NMOS Early voltage is  $V_{An}=10\text{V}$  and PMOS is  $V_{Ap}=20\text{V}$ .  $R_1=R_2=10\text{K}$ ,  $C_1=C_2=C_3=C_4=1\text{pF}$ . Neglect the body effect. Please
- draw the differential mode half circuit and calculate its differential mode gain. (5%)
  - draw the common mode half circuit and calculate its common mode gain. (5%)
  - draw the different mode frequency response. (5%)
  - what do  $R_1$  and  $R_2$  do for differential and common mode operation in this circuit? (5%)

 


Fig. P5

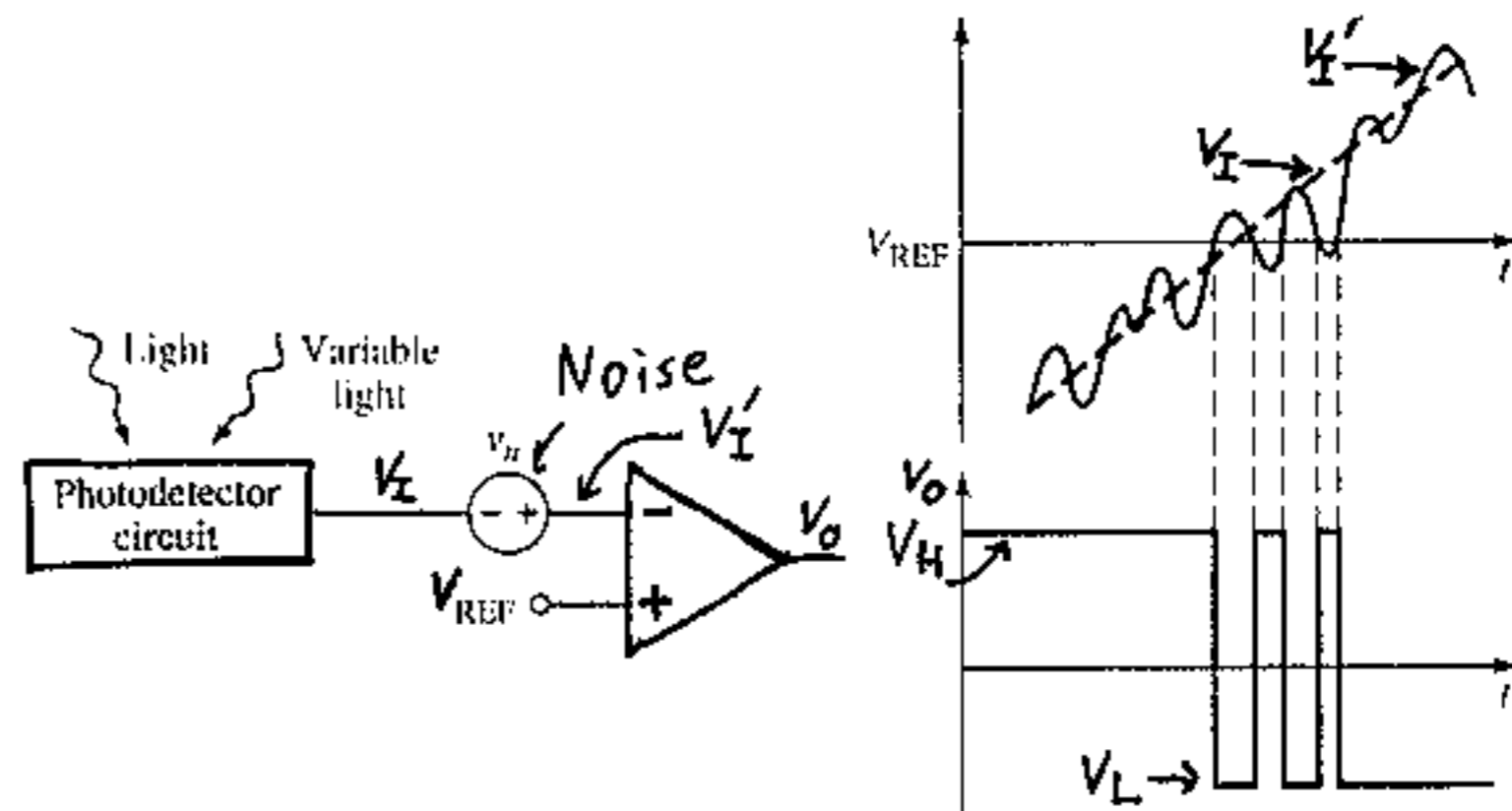


Fig. P6

6. As shown in Fig. P6, a street light system is unstable when noise exists around the threshold. Please redesign this system by using Schmitt trigger.
- Show your design with simple explanation. (10%)
  - If the output of the OP is  $V_H$  or  $V_L$  (Saturation Voltages with  $V_H > 0 > V_L$ ), find the threshold voltages in your design. (10%)
7. (15%) This is the problem about conventional Dynamic Random Access Memory (DRAM).
- Draw the structure of a conventional DRAM cell.
  - How to perform the read operation? (Note that the bus capacitance is greater than that in DRAM cell)
  - If a constant leakage current  $I_{leak}$  exists, and the capacitance of the DRAM cell is  $C_{cell}$ , calculate the refresh period if the power supply and threshold voltage of the NMOS pass transistor is  $V_{DD}$  and  $V_{TN}$ , respectively. ( $\text{Logic-1} \geq V_{DD}/2$ )