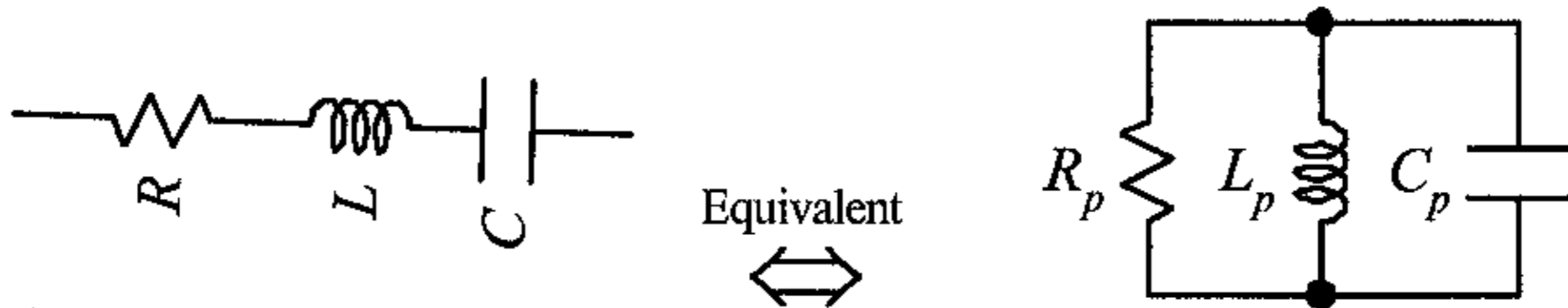


九十二學年度 電機工程學 系(所) \_\_\_\_\_ 甲 \_\_\_\_\_ 組碩士班研究生招生考試


科目 電路學 科號 2304 共 3 頁第 1 頁 \*請在試卷【答案卷】內作答

1. (a) As shown in the following figure, a series  $RLC$  circuit can be transformed into a parallel  $RLC$  circuit with the same impedance. Please use  $R, L, C$  and the angular frequency  $\omega$  to represent  $R_p, L_p,$  and  $C_p$ . (Note: All component values are larger than zero.) (10%)




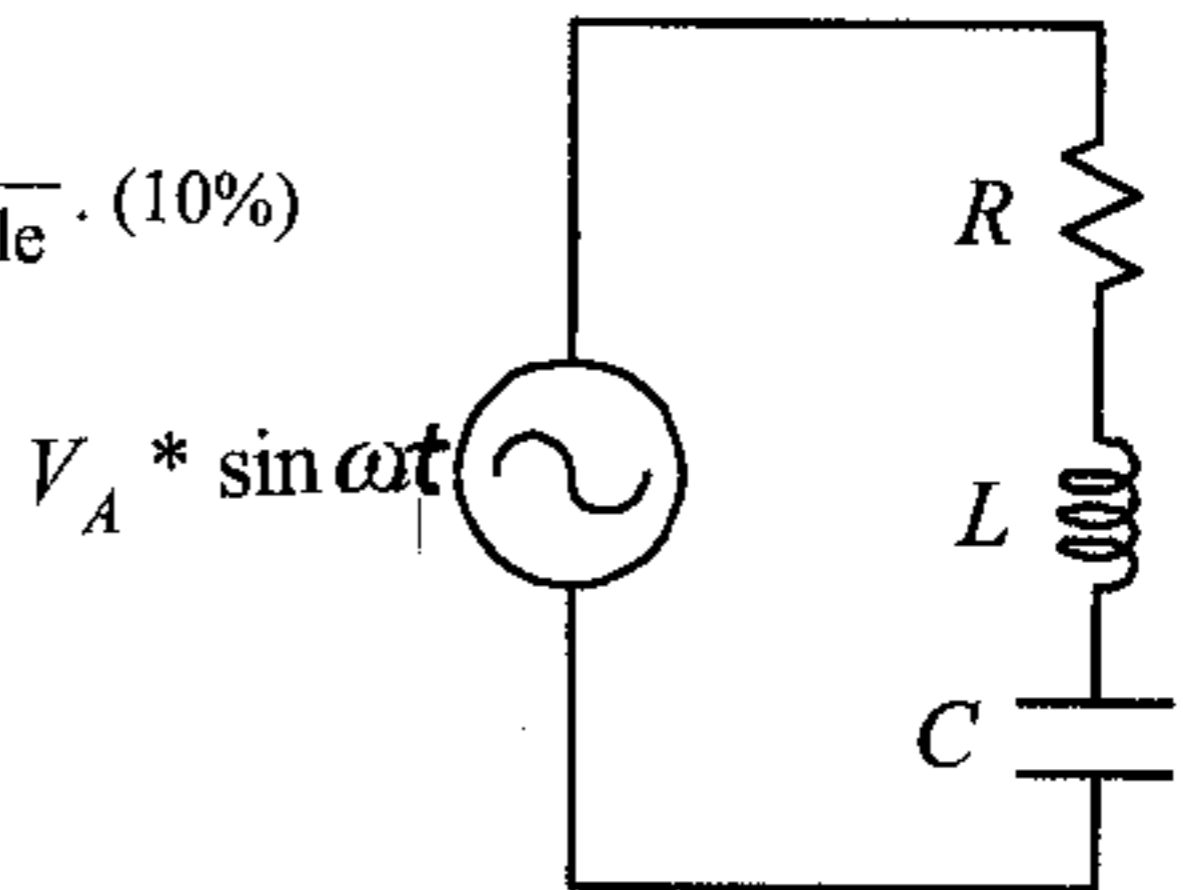- (b) In the following circuit, please find the expression of the quality factor  $Q$  which is defined as

$$Q = 2\pi \cdot \frac{\text{Energy stored in } LC}{\text{Energy consumed by } R \text{ per cycle}} \cdot (10\%)$$



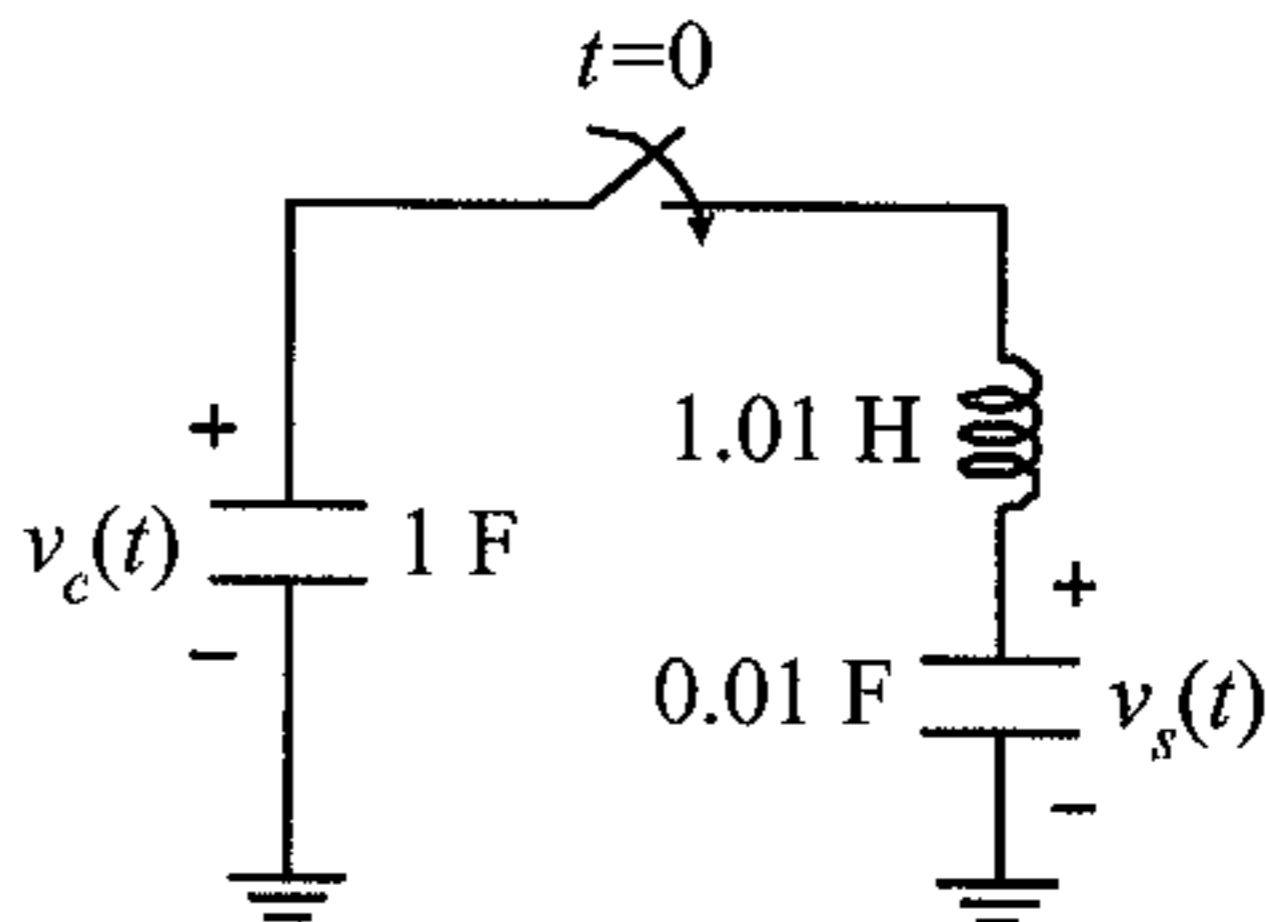
2. In the following circuit, please find the voltage  $v_c(t)$  and  $v_s(t)$  for  $t \geq 0$  where  $v_c(0) = 1$  Volt and  $v_s(0) = 0$  Volt. (Note: The circuit is in steady state before  $t = 0$ .) (10%)



3. For the given circuit,  $v_1 = 120 \cos(100t)u(t)$  V,  $v_2 = 30u(t)$  V, where  $u(t)$  is the unit step function. please find

- (a) time domain representation of the current  $i$  at the steady state.
- (b) the average power consumed by  $R_{load}$  at the steady state.
- (c) the instantaneous power consumed by  $R_{load}$  at the steady state.

(15%)

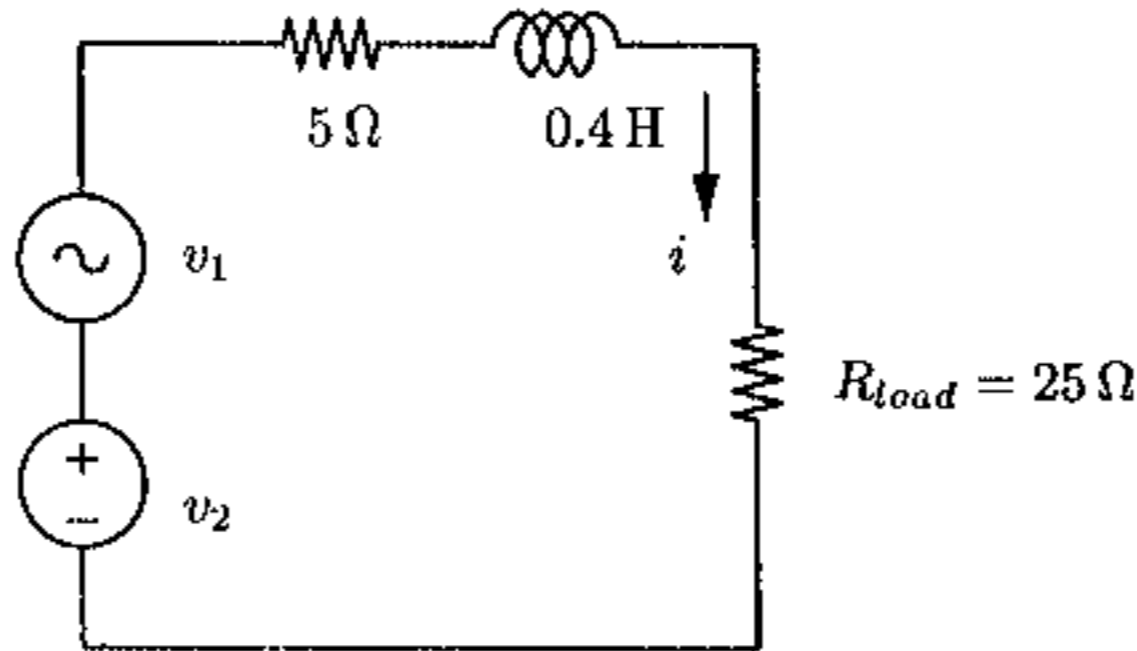


4.

Two linear loads are powered by an AC voltage source as shown. Load 1 consumes 24kW at  $pf = 0.6(\text{lag})$ , and Load 2 consumes 10kVA at  $pf = 0.8(\text{lead})$ .

- (a) Find the equivalent impedance of load 1 and load 2 respectively.
- (b) Find the combined complex power  $S_{total}$  and the combined power factor  $pf_{total}$ .
- (c) Design a compensation scheme to achieve  $pf_{total} = 1.0$ .

(15%)

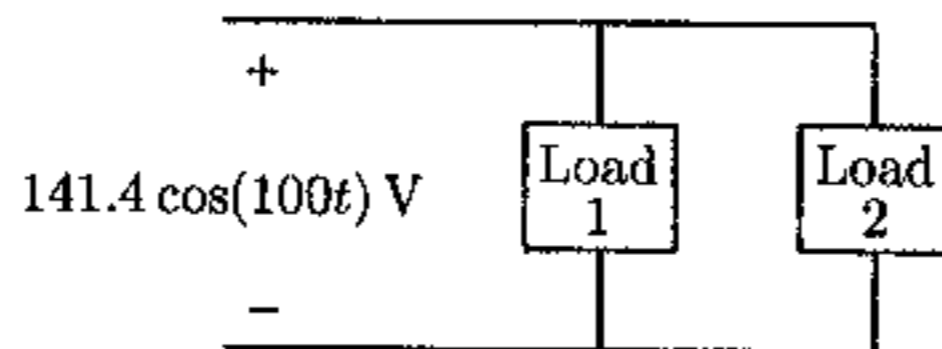

5


The G and H parameters for the resistive two-ports are given as follows:

$$\begin{aligned} H_{11} &= 150 \text{ ohms} & ; & & H_{12} &= -0.05 \\ H_{21} &= -0.10 & ; & & H_{22} &= 0.0001 \text{ mho} \\ G_{11} &= 0.01 \text{ mho} & ; & & G_{12} &= -4.0 \\ G_{21} &= 20.0 & ; & & G_{22} &= 24000 \text{ ohms} \end{aligned}$$

(20%)

Calculate the output voltage  $V_o$  if  $V_g = 109.5$  volt dc. The parameters are defined as follows:
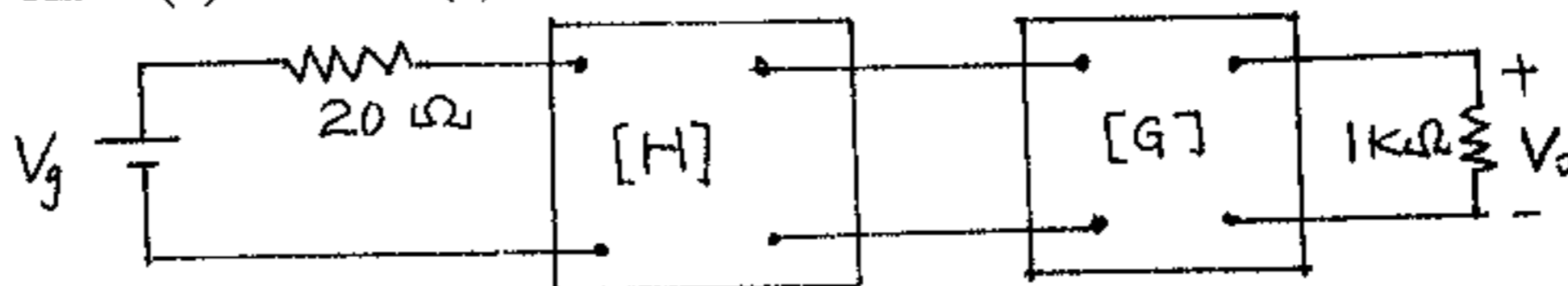
$$\begin{aligned} V(1) &= H_{11} \cdot I(1) + H_{12} \cdot V(2) & ; & & I(1) &= G_{11} \cdot V(1) + G_{12} \cdot I(2) \\ I(2) &= H_{21} \cdot I(1) + H_{22} \cdot V(2) & ; & & V(2) &= G_{21} \cdot V(1) + G_{22} \cdot I(2) \end{aligned}$$



國立清華大學命題紙

九十二學年度 電機工程學 系(所) 甲 組碩士班研究生招生考試

科目 電路學 科號 2304 共 3 頁第 3 頁 \*請在試卷【答案卷】內作答

6. Use the node-voltage to find  $V$  in the following circuit.

(20%)

