
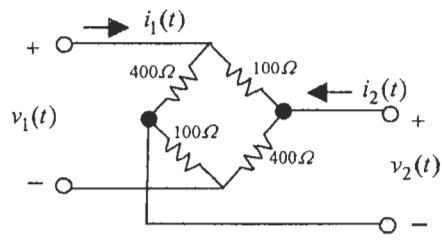


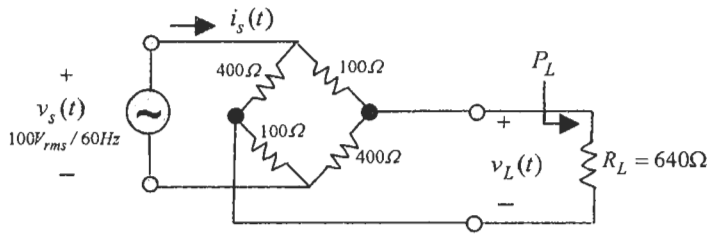
1. (1) Find the z parameters of the given two-port network. (7%)




(2) Now the above network is connected as below to deliver power from source to load. Find the load real power P_L . (7%)



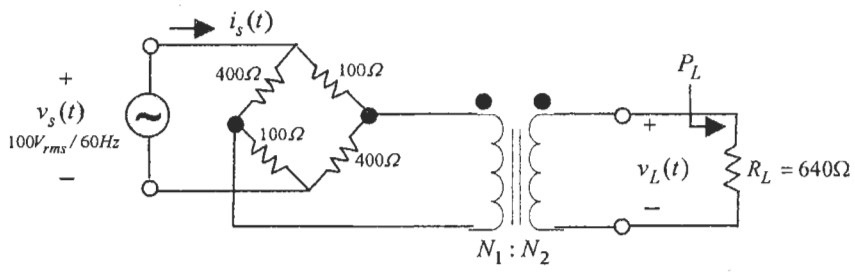(3) If the maximum power transfer is desired, find the transformer turn ratio $N_1 : N_2$ and this maximum load power. (6%)




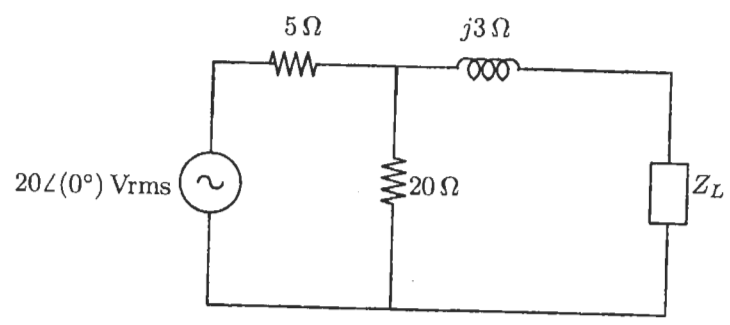2. (a) For the given circuit, please determine the impedance Z_L which results in maximum average power transferred to Z_L .
 (b) Find the real power, reactive power and complex power associated with Z_L .




(10%)

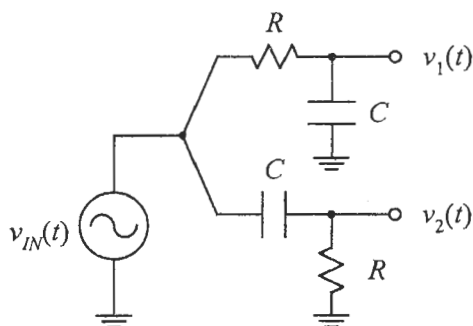3. Assume in the following circuit, the resistance of R is equal to $2\text{ k}\Omega$ and the capacitance of C is equal to 0.5 nF .
- (a). If $v_{IN}(t)$ is an unit step function, i.e., $v_{IN}(t) = 0\text{ V}$ when $t < 0$ and $v_{IN}(t) = 1\text{ V}$ when $t \geq 0$, please calculate $v_1(t)$ and $v_2(t)$. (6%)
- (b). When $v_{IN}(t) = \sin\omega t$, $v_1(t)$ and $v_2(t)$ can be expressed as $A_1 \times \sin(\omega t + \theta_1)$ and $A_2 \times \sin(\omega t + \theta_2)$, respectively. Please find the value ω so that $A_1 = A_2$. Also please calculate the phase difference $(\theta_1 - \theta_2)$ in this condition. (7%)




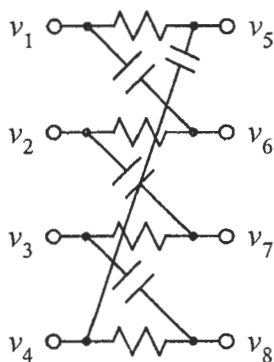4. There is a multi-input/multi-output RC network shown in the following figure. All the resistor values are equal to $50\text{ k}\Omega$ and all the capacitor values are equal to 20 nF . Its inputs are $v_1, v_2, v_3,$ and v_4 . Its outputs are $v_5, v_6, v_7,$ and v_8 .
- (a). If $v_1(t) = \sin(1000 \times t)$, $v_2(t) = \cos(1000 \times t)$, $v_3(t) = -\sin(1000 \times t)$, $v_4(t) = -\cos(1000 \times t)$, please find $v_5, v_6, v_7,$ and v_8 . (6%)
- (b). If $v_1(t) = \sin(1000 \times t)$, $v_2(t) = -\cos(1000 \times t)$, $v_3(t) = -\sin(1000 \times t)$, $v_4(t) = \cos(1000 \times t)$, please find $v_5, v_6, v_7,$ and v_8 . (6%)




5. (a) In a coupled inductor, why is the coupling coefficient k often less than 1.0?
 (b) For a low-pass filter $\frac{p_1}{s+p_1}$ ($p_1 > 0$), why is p_1 often referred to as the 3-db frequency?
 (c) Can you find the phasor representation of $v(t) = e^{-0.01t} \cos(100t)$, ($0 < t < 1.0 \text{ sec}$) (Yes/No)?
 Explain your answer. (10%)

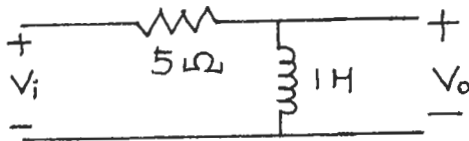6. (a) Find the transfer function of the following circuit where the input and the output are denoted as V_i and V_o respectively. (7%)
 (b) Also find the impulse response of this circuit. (8%)



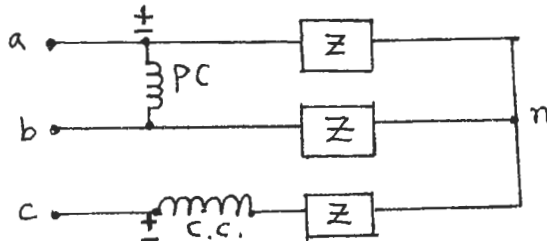7. In the following balanced positive phase sequence three-phase circuit, the three-phase load is known to be $30\text{kW} + j 40\text{kVars}$. If an ideal wattmeter is connected as shown in the circuit where cc and pc denotes the current coil and the potential coil respectively, what is the wattmeter reading? (10%)



8. Assume that the following periodic voltage is applied to a one ohm resistor.
 $V(t) = 30 + 20 \cos 50t + 10 \sin 100t - 5 \cos 150t$ volts
 Calculate the average power delivered to this resistor. (10%)