

國立清華大學 命題紙

95 學年度 電機領域聯合招生 系(所) \_\_\_\_\_ 組碩士班入學考試


科目 電路學 科目代碼 9908 共 3 頁第 1 頁 \*請在【答案卷卡】內作答

1. For the following circuit, assume the values of the resistor  $R$  is  $1\text{ k}\Omega$ , the value of the inductor  $L$  is  $1\text{ mH}$ , and the value of the capacitor  $C$  is  $0.5\text{ nF}$ . The current source  $i_{IN}(t) = 2 \times \sin(10^6 \times t)$  mA and the initial voltage of the capacitor is  $-4\text{ V}$ , i.e.,  $v_C(0) = 4\text{ V}$ .


- (a). Please find the steady-state response of  $v_{OUT}(t)$ . (5%)
- (b). Please find the expressions of  $E_L(t)$  and  $E_C(t)$ , which represent the energy stored in the inductor  $L$  and the capacitor  $C$ , respectively. (6%)
- (c). Assume the quality factor  $Q$  is defined as

$$Q = 2\pi \times \frac{\text{Maximum energy stored in } L \text{ and } C}{\text{Energy consumed by } R \text{ per period}}$$

Please calculate the  $Q$  value. (6%)

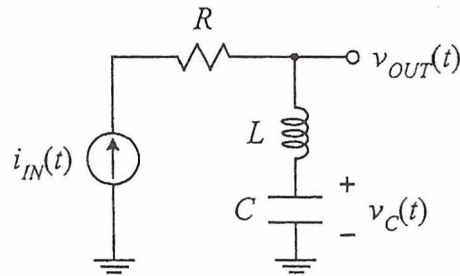

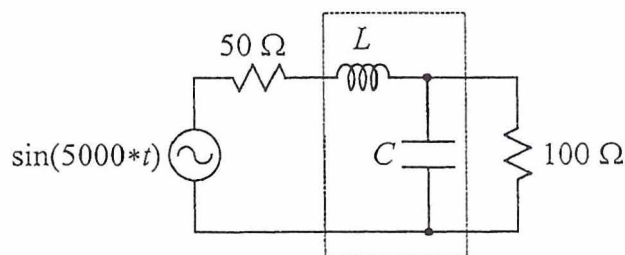2. As shown below, a voltage source with  $50\ \Omega$  output impedance is used to drive a  $100\ \Omega$  loading. In order to deliver the maximum power to the  $100\ \Omega$  loading, a LC circuit is added between the voltage source and the loading. Please find the values of the inductor and capacitor in this LC circuit. (8%)



國立清華大學 命題紙


95 學年度 電機領域聯合招生 系(所) \_\_\_\_\_ 組碩士班入學考試

科目 電路學 科目代碼 9908 共 3 頁第 2 頁 \*請在【答案卷卡】內作答

3. Assume the OPAMP of the given circuit operates in linear range.  $v_s = 10 \cos(10t)u(t)$  V, where  $u(t)$  represents the unit step function. The initial condition of the capacitor is given as  $v_c(t=0) = 0$ .

- (a) Find the complete time domain expression  $v_o(t)$ ;
- (b) Use the phasor analysis technique to find the output voltage in the time domain.
- (c) Are the answers of (a) and (b) the same (yes/no)? Explain their relationship.

(15%)

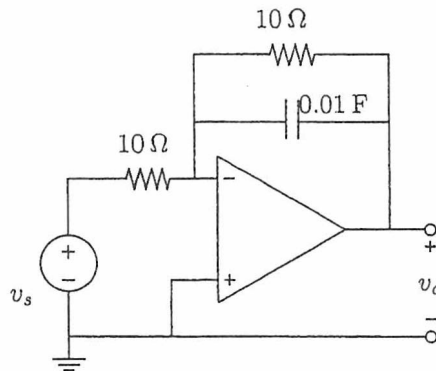

4. (a) Can you find the phasor representation of  $v(t) = \cos(100t) + 3 \cos(200t)$  (Yes/No)? Explain your answer.


(b) If an OPAMP circuit operates in the saturation mode, can this circuit be analyzed by using the superposition technique (Yes/No)? Explain your answer.

(c) Can a light bulb consume only reactive power while emitting light (Yes/No)? Explain your answer.

(15%)

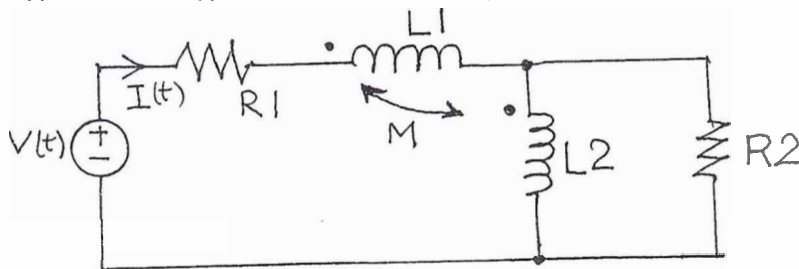5. Given the following circuit,  $L_1=2H$ ,  $L_2=8H$ ,  $M=4H$ ,  $R_1=R_2=2.0$  ohms,

$V(t)=100 \cos(t)$  volts, find the steady state solution of  $I(t)$ . (15%)




國立清華大學 命題紙

95 學年度 電機領域聯合招生 系(所) \_\_\_\_\_ 組碩士班入學考試

科目 電路學 科目代碼 9908 共 3 頁第 3 頁 \*請在【答案卷卡】內作答

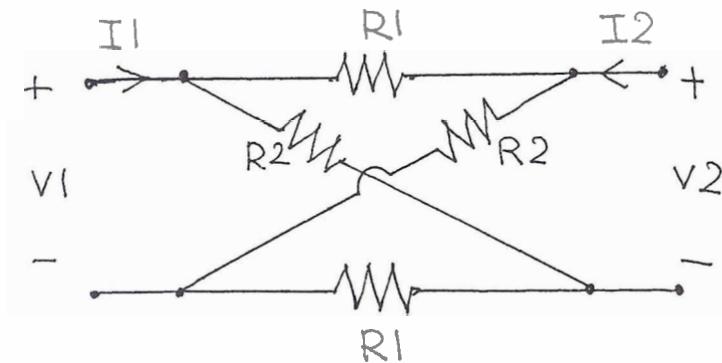6. Find the impedance parameters (i.e.,  $Z_{ij}$ ) of the following linear circuit. (15%)



7. Find the real power  $P$ , reactive power  $Q$ , apparent power  $S$  and power factor of the following three phase load. Assume the balanced three phase voltage source has a line to line voltage of 200 volts and  $Z = 3 + j4$  ohms. (15%)

