


國立清華大學 命題紙

96 學年度 電機領域聯合招生 系(所) _____ 組碩士班入學考試

科目 電路學 科目代碼 9908 共 3 頁第 1 頁 *請在【答案卷卡】內作答

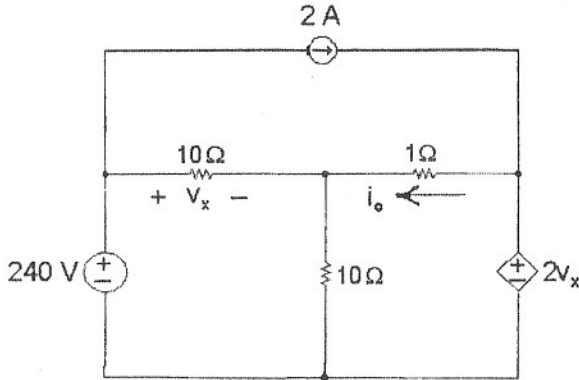1.

Find the power associated with the dependent source in the follow circuit. (10%)



2.


The following dc measurements were made on the two-port network shown below. Which parameters are easiest to find from the measurements? (3%) Find the values of them. (12%)

Open-circuit Port 2

Apply $V_1 = 20 \text{ mV}$
 Measure $I_1 = 0.25 \text{ } \mu\text{A}$
 Measure $V_2 = -5 \text{ V}$

Short-circuit Port 2

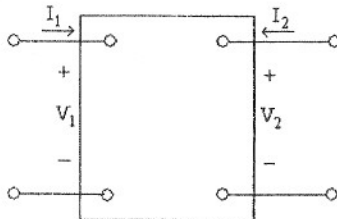
Apply $V_1 = 10 \text{ V}$
 Measure $I_1 = 200 \text{ } \mu\text{A}$
 Measure $I_2 = 50 \text{ } \mu\text{A}$



$$\begin{aligned}
 V_1 &= z_{11}I_1 + z_{12}I_2 & I_1 &= y_{11}V_1 + y_{12}V_2 & V_1 &= h_{11}I_1 + h_{12}V_2 & I_1 &= g_{11}V_1 + g_{12}I_2 & V_1 &= a_{11}V_2 - a_{12}I_2 & V_2 &= b_{11}V_1 - b_{12}I_1 \\
 V_2 &= z_{21}I_1 + z_{22}I_2 & I_2 &= y_{21}V_1 + y_{22}V_2 & I_2 &= h_{21}I_1 + h_{22}V_2 & V_2 &= g_{21}V_1 + g_{22}I_2 & I_1 &= a_{21}V_2 - a_{22}I_2 & I_2 &= b_{21}V_1 - b_{22}I_1
 \end{aligned}$$

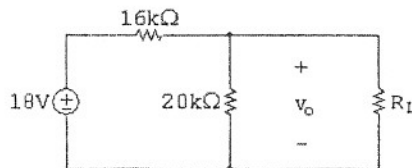3.

Find the no-load voltage (5%) and load voltage (5%) for $R_L = 5 \text{ k}\Omega$.




國立清華大學 命題紙


96 學年度 電機領域聯合招生 系(所) _____ 組碩士班入學考試

科目 電路學 科目代碼 9908 共 3 頁第 2 頁 *請在【答案卷卡】內作答

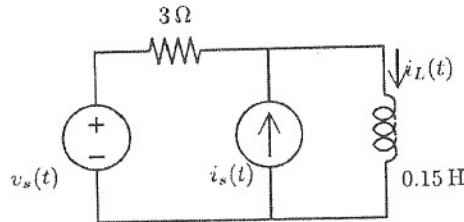
4. (15%) Use the superposition technique, find the inductor current $i_L(t)$ at steady state. $v_s(t) = 5 \cos(26.66t)$ V, $i_s(t) = 10 \sin(20t)$ A. Note $\cos(53.1^\circ) \approx 0.6$.



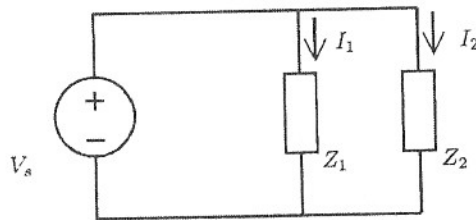5. (20%) In the given circuit, $V_s = 120 \angle (10^\circ)$ V(rms), $I_1 = 2 \angle (40^\circ)$ A(rms), $I_2 = 3 \angle (-35^\circ)$ A(rms).
- Find the impedances Z_1 and Z_2 .
 - Calculate the complex power, the average power, and the reactive power of Z_1 and Z_2 respectively.
 - To compensate the power factor of the total load (Z_1 and Z_2) into 1.0, what component is needed (L or C)? Please calculate its impedance.



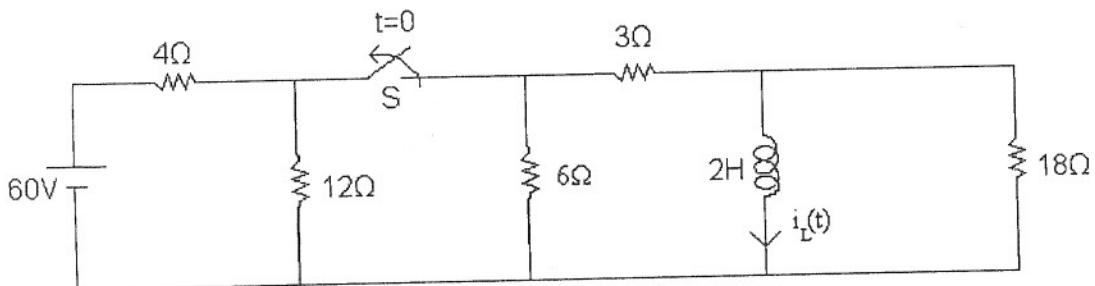6. The following circuit has been in steady state for a long time at $t=0$. The switch S is opened at $t=0$. Find $i_L(0^+)$ and $i_L(t)$ for $t \geq 0^+$. (15%)



7. Find the steady state solution of $V_x(t)$ and $i_2(t)$ for the following circuit. Given $L_1=L_2=M=4H$, $C=1F$, $V_{s1}(t) = V_m \cos(t + \theta_1)$ volts, $V_{s2}(t) = 10 \cos(t + 90^\circ)$ volts where $V_m \cos \theta_1 + j V_m \sin \theta_1 = 4 + j20$. (15%)

