
九十三學年度 丁 3 斗 系 (所) \_\_\_\_\_\_ 組碩士班入學考試 科目 電 3 學 \_\_\_\_\_ 科號 4/02 共 3 頁第 1 頁 \*請在試卷【答案卷】內作答
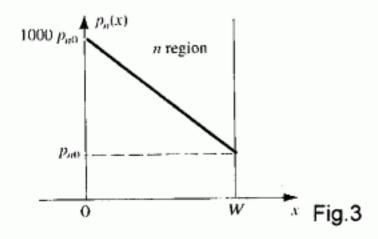
## (請注意!! 答案之順序務必按題號順序)

- Sketch a 2<sup>20</sup>-bit memory chip organized as an array of 2<sup>10</sup> rows X2<sup>10</sup> columns. This illustration should include bit lines, word lines, sense amplifiers/drivers, row decoders, and column decoders. (10 pts)
- 2. Is a CMOS inverter ratio or ratioless gate ? What are the advantages ? For the matching purpose in CMOS inverter, what is the relation among (W/L)p, (W/L)n, mobility  $\mu_n$ , and  $\mu_p$ ? (15 pts)
- 3. Holes are being injected into a region of n-type silicon. In the steady state, the excess-hole concentration profile is shown in Fig.3. If  $N_D$ =  $10^{16}$ /cm³,  $n_i$ =  $1.5X10^{10}$ /cm³, Dp= 12 cm²/s, and W= 5  $\mu$  m, find the current density that will flow in the x direction. (10 pts)



4. In the Fig.4, vs is a small signal with zero average value. If  $\beta$ = 50, find R<sub>in</sub> and gain vo/vs. (10 pts)

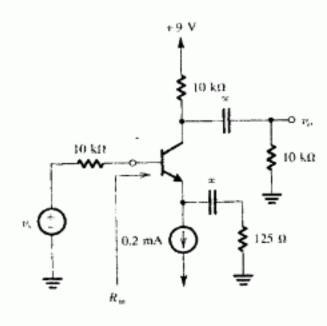


Fig.4

九十三學年度 フラナ 系 (所) <u>ブ</u>組碩士班入學考試 科目 **で 子 学** 科號 4/02 共 3 頁第 2 頁 \*請在試卷【答案卷】內作答

 By using feedback analysis in Fig.5, find the voltage gain Vo/Vs, R<sub>in</sub>, and R<sub>out</sub> of the circuit for device with V<sub>t</sub>= 2V and K<sub>n</sub>'(W/L)= 0.5 mA/V<sup>2</sup>.(15 pts)

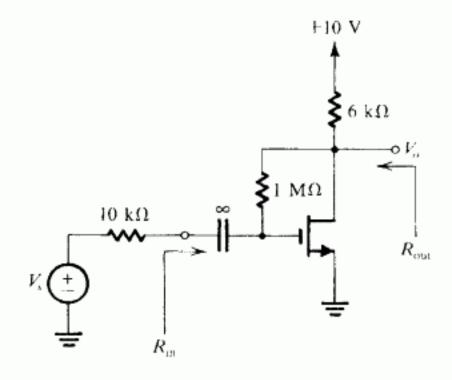


Fig.5

In Fig. 6, Q<sub>1</sub> and Q<sub>2</sub> have equal g<sub>m</sub> and r<sub>o</sub>. If the output resistance of I<sub>BIAS2</sub> is r<sub>o</sub> and the total capacitance at output node is C<sub>L</sub>, find the voltage gain Vo/Vi and the dominant pole frequency ω<sub>H</sub>. (16 pts)

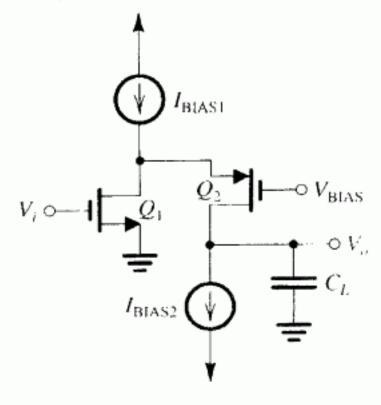


Fig.6

九十三學年度 エ 手斗 系 (所) \_\_\_\_ J \_\_ 組碩士班入學考試 科目 \_\_\_ 全 子 写 \_\_\_ 科號 4/02 共 3 頁第 3 頁 \*請在試卷【答案卷】內作答

7. The equivalent circuit of a quartz oscillator is shown in Fig.7. Why is the oscillation frequency  $\omega_o$  very stable? And find  $\omega_o$ . (10 pts)

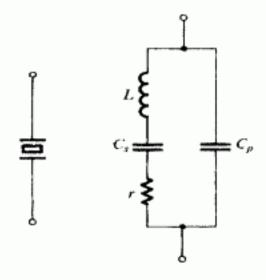


Fig.7

8. For the case of all devices with equal magnitude of early voltage V<sub>A</sub> in Fig.8, find the voltage gain Vo/Vi in terms of K<sub>n</sub>', (W/L)<sub>n</sub>, I<sub>REF</sub>, and V<sub>A</sub>. Is the circuit affected by the body effect? And why? (14 pts)

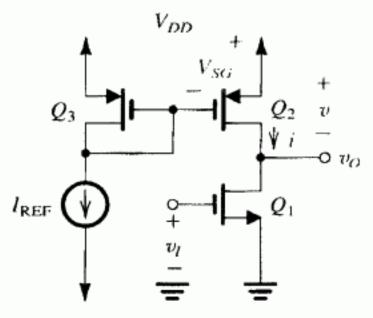


Fig.8